

1. (a) 5 nodes
- (b) 6 elements
- (c) 6 branches

2. (a) 4 nodes;
- (b) 7 elements;
- (c) 7 branches (we omit the  $2\ \Omega$  resistor as it is not associated with a path in our definition)

3. (a) 4 nodes
- (b) path, yes; loop, no
- (c) path, no; loop, no

4. (a) 6 elements;
- (b) path, yes; loop, no.
- (c) path, yes; loop, no.

5. (a) 4 nodes
- (b) 4 elements
- (c) 4 branches
- (d) i) neither; ii) path only;
- iii) both path and loop; iv) neither ('c' encountered twice).

6. The parallel-connected option would allow most of the sign to still light even if one or more individual bulbs burn out. For that reason, it would be more useful to the owner.

7. By KCL,  $i_A - i_B + i_C + i_D - i_E = 0$ . Thus,


(a)  $1 - i_B + 3 - 2 - 0 = 0$  so  $i_B = 2$  A.

(b)  $-1 - (-1) - 1 - 1 - i_E = 0$  so  $i_E = -2$  A.

8. (a) By KCL,  $7 = 6 + I$  so  $I = 1 \text{ A}$
- (b) By KCL,  $2 = 3 + I + 3$  so  $I = -4 \text{ A}$
- (c) No *net* current can flow through the resistor or KCL would be violated.

Hence,  $I = 0$ .

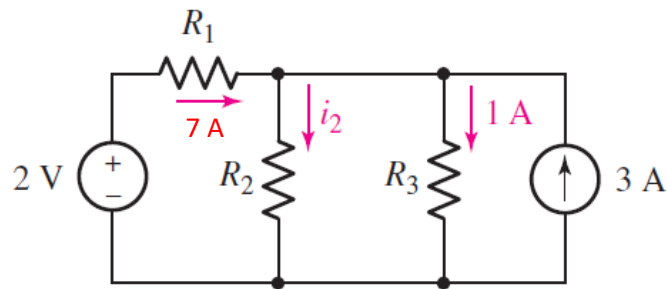9. We note that KCL requires that if 7 A flows out of the “+” terminal of the 2 V source, it flows left to right through  $R_1$ . Equating the currents into the top node of  $R_2$  with the currents flowing out of the same node, we may write




$$7 + 3 = i_2 + 1$$

or

$$i_2 = 10 - 1 = \boxed{9 \text{ A}}$$

10. By KCL,  $i_A + i_B + i_C = i_{\text{battery}} + i_{\text{sign}}$ . Hence,  $i_{\text{battery}} = i_A + i_B + i_C - i_{\text{sign}} = 8.3 \text{ A}$ .

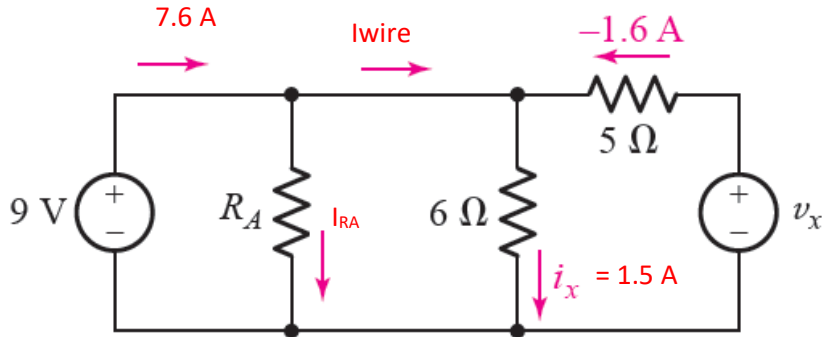11. We can determine  $R_A$  from Ohm's law if either the voltage across, or the current through the element is known. The problem statement allows us to add labels to the circuit diagram:



Applying KCL to the common connection at the top of the  $6\ \Omega$  resistor,  
 $I_{wire} = 1.5 - (-1.6) = 3.1\text{ A}$

Applying KCL to the top of  $R_A$  then results in

$$I_{RA} = 7.6 - I_{wire} = 7.6 - 3.1 = 4.5\text{ A.}$$

Since the voltage across  $R_A = 9\text{ V}$ , we find that  $R_A = 9/4.5 = \boxed{2\ \Omega}$

12. By KCL,

$$I_B + I_C = I_E \quad [1].$$

Given that  $I_C = 1.5 \text{ mA}$ , we are left with one equation in two unknowns.

Noting that  $I_C = 50 I_B$ , we may rewrite Eq. [1] as

$I_C/50 + I_C = I_E$ . Solving,  $I_E = 1.53 \text{ mA}$ , and  $I_B = I_C/50 = 0.03 \text{ mA}$ .


13. By inspection,  $I_3 = -5V_x$  due to the action of the dependent source.

$$V_x = (2 \times 10^{-3})(4.7 \times 10^3) = 9.4 \text{ V}$$

Hence,  $I_3 = -47 \text{ A}$

14. With finite values of  $R_1$  some value of current  $I$  will flow out of the source and through the left-most resistor. If we allow some small fraction of that current  $kI$  ( $k < 1$ ) to flow through the resistor connected by a single node, to where does the current continue? With nowhere for the current to go, KCL is violated. At best we must imagine an equal current flowing the opposite direction, yielding a **net** current of zero. Consequently,  $V_x$  must be zero.

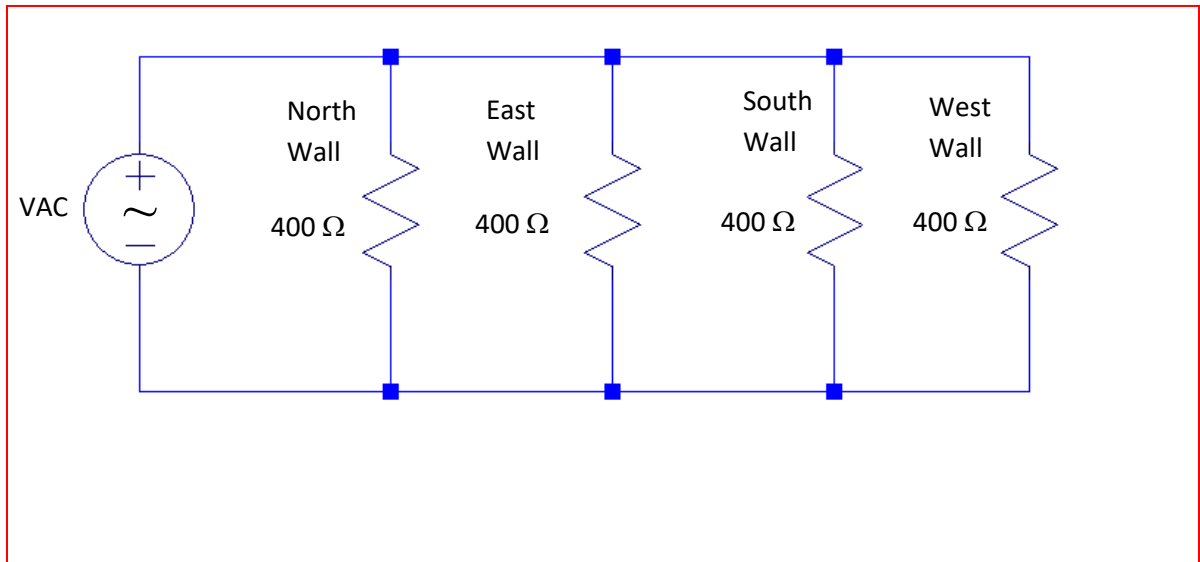15. The order of the resistors in the schematic below is unimportant.



16. (a)  $-v_1 + v_2 - v_3 = 0$   
Hence,  $v_1 = v_2 - v_3 = 0 + 17 = 17 \text{ V}$
- (d)  $v_1 = v_2 - v_3 = -2 - 2 = -4 \text{ V}$
- (e)  $v_2 = v_1 + v_3 = 7 + 9 = 16 \text{ V}$
- (f)  $v_3 = -v_1 + v_2 = 2.33 - 1.70 = 0.63 \text{ V}$

17. (a) By KVL,  $+9 + 4 + v_x = 0$

Therefore  $v_x = -13 \text{ V}$

From Ohm's law,  $i_x = v_x/7 = -13/7 = -1.86 \text{ A}$

(b) By KVL,  $+2 + (-7) + v_x = 0$ . Thus,  $v_x = 5 \text{ V}$ .

Using Ohm's law,  $i_x = v_x/8 = 625 \text{ mA}$ .

18. (a) Combining KVL and Ohm's law,

$$-1 + 2 + 2i - 5 + 10i = 0$$

Hence,  $12i = 4$  so  $i = 333 \text{ mA}$

(b) Again combining KVL and Ohm's law,

$$10 + 2i - 1.5 + 1.5 + 2i + 2i + 2 + 2i - 1 + 2i = 0$$

Hence,  $i = -11/10$  so  $i = -1.1 \text{ A}$

19. From KVL,  $+4 - 23 + v_R = 0$  so  $v_R = 23 - 4 = 19$  V

Also,  $-v_R + 12 + 1.5 - v_2 - v_3 + v_1 = 0$

or  $-19 + 12 + 1.5 - v_2 - 1.5 + 3 = 0$

Solving,  $v_2 = -4$  V

20.  $V_{\text{dep}} = V_2 - 1000I_C - 1000I_C.$

With  $V_2 = 15 \text{ V}$ ,  $I_C = 50I_B = 50(20 \times 10^{-6}) = 0.001 \text{ A}$

Therefore,


$$V_{\text{dep}} = 15 - 2000(0.001) = 13 \text{ V.}$$

21. We apply KCL/KVL and Ohm's law alternately, beginning with the far left. Knowing that 500 mA flows through the  $7.3 \Omega$  resistor, we calculate 3.65 V as labelled below. Then application of KVL yields  $2.3 - 7.3 = -1.35$  V across the  $1 \Omega$  resistor.

This tells us that  $-1.35/1 = -1.35$  A flows downward through the  $1 \Omega$  resistor. KCL now tells us that  $0.5 - (-1.35) = 1.85$  flows through the top  $2 \Omega$  resistor. Ohm's law dictates a voltage of 3.7 V across this resistor in this case.

Application of KVL determines that  $-(-1.35) + 3.7 + v_2 = 0$  or -5.05 V appears across the right-most  $2 \Omega$  resistor, as labelled below. Since this voltage also appears across the current source, we know that

$$V_x = -5.05 \text{ V}$$

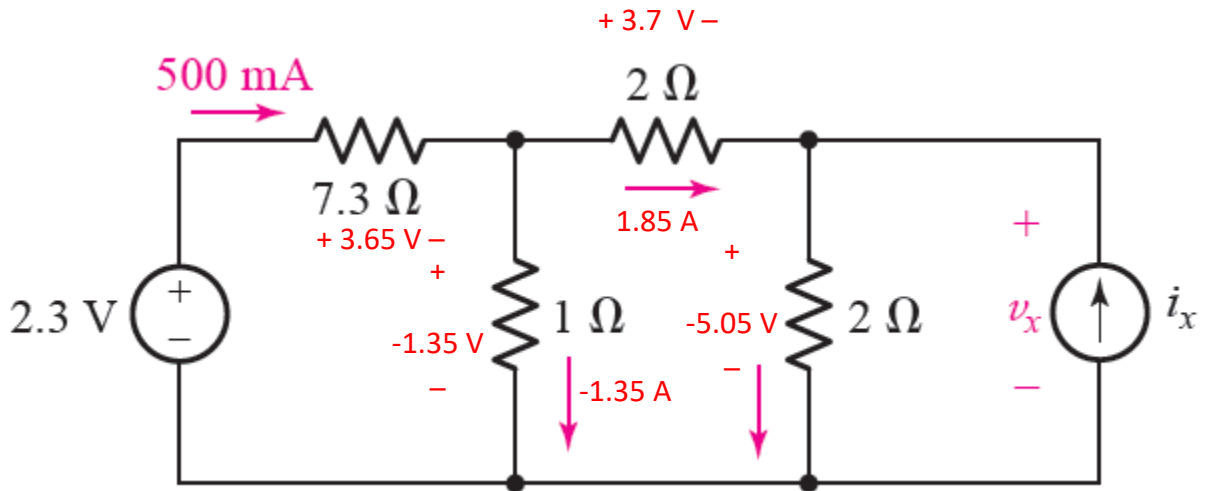

22. (a) By KVL,  $-v_s + v_1 + v_2 = 0$  [1]  
Define a clockwise current  $I$ . Then  $v_1 = IR_1$  and  $v_2 = IR_2$ .

Hence, Eq. [1] becomes

$$-v_s + IR_1 + IR_2 = 0$$

Thus,  $v_s = (R_1 + R_2)I$  and  $I = v_1/R_1$

so  $v_s = (R_1 + R_2)v_1/R_1$  or  $v_1 = v_s R_1 / (R_1 + R_2)$ . QED

Similarly,  $v_2 = IR_2$  so we may also write,

$$v_s = (R_1 + R_2)v_2/R_2 \text{ or } v_2 = v_s R_2 / (R_1 + R_2). \quad \text{QED}$$

(Proof, so final answer was given to begin with.)

(b)  $R_1 > 0$ .

23. (a) By inspection:

$$v_1 = 2 \text{ V}; \quad v_2 = 2 \text{ V};$$

$$i_2 = 2/6 = 333 \text{ mA}$$

$$i_3 = 5v_1 = 10 \text{ A}$$

$$i_1 = i_2 + i_3 = 10.33 \text{ A}$$

$$v_4 = v_5 = 5i_2 = 5(1/3) = 5/3 \text{ V}$$

$$i_5 = (5/3)/5 = 333 \text{ mA}$$

$$i_3 = i_4 + i_5 \quad \text{therefore} \quad i_4 = i_3 - i_5 = 10 - 1/3 = 9.67 \text{ A}$$

$$-v_2 + v_3 + v_4 = 0 \quad \text{therefore} \quad v_3 = v_4 + v_2 = 6/3 = 333 \text{ mV}$$

(b) Using the passive sign convention (assuming all elements absorb power):

$$v_1(-i_1) + v_2(i_2) + v_3(i_3) + v_4(i_4) + v_5(i_5) = 0 \quad (\text{should be true, within rounding error}).$$

$$= -62/3 + 2/3 + 10/3 + 145/9 + 5/9 = 0, \text{ so true.}$$

24. Define the current  $I$  flowing out of the “+” reference terminal of the 5 V source. This current also flows through the 100  $\Omega$  and 470  $\Omega$  resistors since no current can flow into the input terminals of the op amp.

$$\text{Then, } -5 + 100I + 470I + v_{\text{out}} = 0 \quad [1]$$

Further, since  $V_d = 0$ , we may also write

$$-5 + 100I = 0 \quad [2]$$

$$\text{Solving, } V_{\text{out}} = 5 - 570I = 5 - 570(5/100) = \boxed{-23.5 \text{ V}}$$

25. With a clockwise current  $i$ , KVL yields

$$-(-8) + (1)i + 16 + 4.7i = 0$$

$$\text{Therefore, } i = -(16 - 8)/5.7 = \boxed{-4.21 \text{ A}}$$

Absorbed power:

$$\text{Source vs1: } +(-8)(+4.21) = \boxed{-33.68 \text{ W}}$$

$$\text{Source vs2: } (16)(-4.21) = \boxed{-67.36 \text{ W}}$$

$$\text{R1: } (4.21)^2(1) = \boxed{17.21 \text{ W}}$$

$$\text{R2: } (4.21)^2(4.7) = \boxed{83.30 \text{ W}}$$

Check: The sum of the above 'absorbed' powers = -0.02, which is within rounding error of zero, as expected.

26. Define a clockwise current  $I$ . Then, KVL yields

$$-12 + 2i + 3i + 5i + 2 + I - 4 = 0$$

$$\text{Hence, } I = 14/11 = 1.27 \text{ A.}$$

Using the passive sign convention to compute power absorbed:

$$P_{12V} = (12)(-1.27) = -15.24 \text{ W}$$

$$P_{2\Omega} = 2i^2 = 3.23 \text{ W}$$

$$P_{3\Omega} = 3i^2 = 4.84 \text{ W}$$

$$P_{5\Omega} = 5i^2 = 8.06 \text{ W}$$

$$P_{2V} = 2(i) = 2.54 \text{ W}$$

$$P_{4V} = 4(-i) = -5.8 \text{ W}$$

$$P_{1\Omega} = (1)i^2 = 1.61 \text{ W}$$

Summing these yields  $-0.04 \text{ W}$ , which is within rounding error of zero, as expected.

27. Define a clockwise current  $I$

Then invoking KVL and Ohm's law we may write

$$500I - 2 + 1000I + 3v_x + 2200I = 0$$

Since  $v_x = -500I$ , the above equation can be recast as

$$500I - 2 + 1000I - 1500I + 2200I = 0$$

Solving,  $I = 2/2200 = 909.1 \mu\text{A}$

#### ABSORBED POWER

|                |            |                       |
|----------------|------------|-----------------------|
| 500 $\Omega$ : | $500(I^2)$ | = 413.2 $\mu\text{W}$ |
|----------------|------------|-----------------------|

|             |           |             |
|-------------|-----------|-------------|
| 2 V source: | $(2)(-I)$ | = -1.818 mW |
|-------------|-----------|-------------|

|                |               |                       |
|----------------|---------------|-----------------------|
| 1 k $\Omega$ : | $(1000)(I^2)$ | = 826.5 $\mu\text{W}$ |
|----------------|---------------|-----------------------|

|             |                   |             |
|-------------|-------------------|-------------|
| Dep source: | $[(3)(-500I)](I)$ | = -1.240 mW |
|-------------|-------------------|-------------|

|                  |               |            |
|------------------|---------------|------------|
| 2.2 k $\Omega$ : | $(2200)(I^2)$ | = 1.818 mW |
|------------------|---------------|------------|

28. (a) By KVL,  $-12 + 27ix + 33ix + 13ix + 2 + 19ix = 0$   
 Hence,  $ix = 10/92 = 108.7 \text{ mA}$

| Element     | $P_{\text{absorbed}}$ | (W)    |
|-------------|-----------------------|--------|
| 12 V        | $(12)(-0.1087) =$     | -1.304 |
| 27 $\Omega$ | $(27)(0.1087)^2 =$    | 0.3190 |
| 33 $\Omega$ | $(33)(0.1087)^2 =$    | 0.3899 |
| 13 $\Omega$ | $(13)(0.1087)^2 =$    | 0.1536 |
| 19 $\Omega$ | $(19)(0.1087)^2 =$    | 0.2245 |
| 2 V         | $(2)(0.1087) =$       | 0.2174 |

- (b) By KVL,  $-12 + 27ix + 33ix + 4v_1 + 2 + 19ix = 0$   
 and  $v_1 = 33ix$ . Solving together,  $ix = 10/211 = 47.39 \text{ mA}$

| Element     | $P_{\text{absorbed}}$ (W) |
|-------------|---------------------------|
| 12 V        | -0.5687                   |
| 27 $\Omega$ | 0.06064                   |
| 33 $\Omega$ | 0.07411                   |
| Dep source  | 0.2964                    |
| 19 $\Omega$ | 0.04267                   |
| 2 V         | 0.09478                   |

- (c) By KVL,  $-12 + 27ix + 33ix + 4ix + 2 + 19ix + 2 = 0$   
 Solving,  $ix = 10/83 = 120.5 \text{ mA}$

| Element     | $P_{\text{absorbed}}$ (W) |
|-------------|---------------------------|
| 12 V        | -1.446                    |
| 27 $\Omega$ | 0.3920                    |
| 33 $\Omega$ | 0.4792                    |
| Dep source  | 0.05808                   |
| 19 $\Omega$ | 0.2759                    |
| 2 V         | 0.2410                    |

29. A simple KVL equation for this circuit is

$$-3 + 100I_D + V_D = 0$$

Substituting in the equation which related the diode current and voltage,

$$-3 + (100)(45 \times 10^{-9}) \left( e^{V_D / 27 \times 10^{-3}} - 1 \right)$$

Solving either by trial and error or using a scientific calculator's equation solver,

$$V_D = 359 \text{ mV}$$

which then allows us to use the diode equation to compute  $I_D = 26.38 \text{ mA}$

30. (a) KCL yields  $3 - 7 = i_1 + i_2$

or,  $-4 = v/4 + v/2$

Solving,  $v = -5.333 \text{ V}$

Thus,  $i_1 = v/4 = -1.333 \text{ A}$  and  $i_2 = v/2 = -2.667 \text{ A}$

(b)

**Element**      **Absorbed Power**

3 A     $(-5.333)(-3) = 16.00 \text{ W}$

7 A     $(-5.333)(7) = -37.33 \text{ W}$

4  $\Omega$      $(4)(-1.333)^2 = 7.108 \text{ W}$

2  $\Omega$      $(2)(-2.667)^2 = 14.23 \text{ W}$

31. Consider the currents flowing INTO the top node. KCL requires

$$-2 - i_1 - 3 - i_2 = 0$$

$$\text{Or } i_1 + i_2 = -5 \quad [1]$$

Also,  $i_1 = v/10$  and  $i_2 = v/6$  so Eq. [1] becomes

$$v/10 + v/6 = -5$$

$$\text{Solving, } v = \boxed{-18.75 \text{ V}}$$

$$\begin{aligned} \text{Thus the power supplied by the } -2 \text{ A source is } (-2)(-18.75) &= \boxed{37.5 \text{ W}} \\ \text{and the power supplied by the } 3 \text{ A source is } -(3)(-18.75) &= \boxed{56.25 \text{ W}} \end{aligned}$$

32. Define  $i_x$  as the current through X, pointing downward.  
By KCL,

$$1 - v/5 - i_x - v/5 + 2 = 0$$

or

$$3 - (2/5)v - i_x = 0$$

- (a) The current source sets  $i_x = 2$  A.

$$\text{Thus, } v = (3 - i_x)(5/2) = 2.5 \text{ V}$$

- (b)  $v = 2$  V, by inspection.

- (c)  $i_x = 2$  V therefore

$$3 - (2/5)v - 2v = 0$$

Solving,

$$v = 15/12 \text{ V} = 1.25 \text{ V}$$

33. Summing the currents flowing into the top node, KCL yields

$$-v/1 + 3ix + 2 - v/3 = 0 \quad [1]$$

Also,  $ix = -v/3$ . Substituting this into Eq. [1] results in

$$-v - v + 2 - v/3 = 0$$

Solving,  $v = 6/7 \text{ V} \quad (857 \text{ mV})$

The dependent source supplies power  $= (3ix)(v)$   
 $= (3)(-v/3)(v) = -36/49 \text{ W} \quad (-735 \text{ mW})$

The 2 A source supplies power  $= (2)(v) = 12/7 \text{ W} = (1.714 \text{ W})$

34. Define the center node as +v; the other node is then the reference terminal.

$$\text{KCL yields } 3 \times 10^{-3} - 5 \times 10^{-3} = \frac{v}{1000} + \frac{v}{4700} + \frac{v}{2800}$$

Solving,  $v = -1.274 \text{ V}$

| (a) R  | P <sub>absorbed</sub> |
|--------|-----------------------|
| 1 kΩ   | 1.623 mW              |
| 4.7 kΩ | 345.3 μW              |
| 2.8 kΩ | 579.7 μW              |

| (b) Source | P <sub>absorbed</sub>                        |
|------------|--|
| 3 mA       | $(v)(3 \times 10^{-3}) = -3.833 \text{ mW}$  |
| 5 mA       | $(v)(-5 \times 10^{-3}) = +6.370 \text{ mW}$ |

|     |   |
|-----|---|
| (c) | $\sum P_{\text{absorbed}} = 2.548 \text{ mW}$                 |
|     | $\sum P_{\text{supplied}} = 2.548 \text{ mW}$                 |
|     | Thus, $\sum P_{\text{supplied}} = \sum P_{\text{absorbed}}$ . |

35. By KVL,  $v_{eq} = v_1 + v_2 - v_3$

(a)  $v_{eq} = 0 - 3 - 3 = -6 \text{ V};$

(b)  $v_{eq} = 1 + 1 - 1 = 1 \text{ V};$

(c)  $v_{eq} = -9 + 4.5 - 1 = -5.5 \text{ V}$


36. KCL requires that  $i_{eq} = i_1 - i_2 + i_3$

$$(a) \ i_{eq} = 0 + 3 + 3 = 6A$$

$$(b) \ i_{eq} = 1 - 1 + 1 = 1A$$

$$(c) \ i_{eq} = -9 - 4.5 + 1 = -12.5A$$

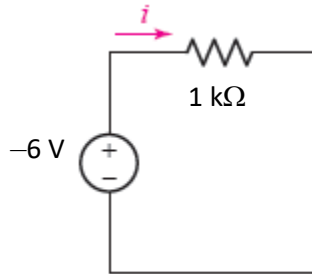37. The voltage sources are in series, hence they may be replaced with  $v_{eq} = -2 + 2 - 12 + 6 = -6$  V. The result is the circuit shown below:




Analyzing the simplified circuit,  $i = -6/1000 =$  -6 mA

38. We may first reduce the series connected voltage sources, or simply write a KVL equation around the loop as it is shown:

$$+2 + 4 + 7i + v_1 + 7i + 1 = 0$$

Setting  $i = 0$ ,  $v_1 = \boxed{-7 \text{ V}}$

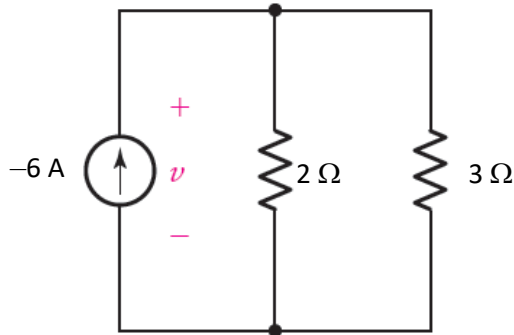39. The current sources are combined using KCL to obtain  $i_{eq} = 7 - 5 - 8 = -6$  A. The resulting circuit is shown below.



(a) KCL stipulates that  $-6 = \frac{v}{2} + \frac{v}{3}$ .

Solving,  $v = -36/5$  V

(b)  $P_{\text{supplied}}$  by equivalent source =  $(v)(-6) = 43.2$  W

| Source     | $P_{\text{supplied}}$ (W) |
|------------|---------------------------|
| 7 A source | $(7)(-36/5) = -50.4$ W    |
| 5 A source | $(-5)(-36/5) = 36$ W      |
| 8 A source | $(-8)(-36/5) = 57.6$ W    |
|            | $43.2$ W so confirmed.    |

40. We apply KCL to the top node to write


$$1.28 - 2.57 = v/1 + I_s + v_s/1$$

Setting  $v = 0$ , we may solve our equation to obtain  $I_s = -1.29 \text{ A}$

41. (a) Employing KCL, by inspection  $I_x = 3 \text{ A}; V_y = 3 \text{ V}$

(b) Yes. Current sources in series must carry the same current. Voltage sources in parallel must have precisely the same voltage.

(c)

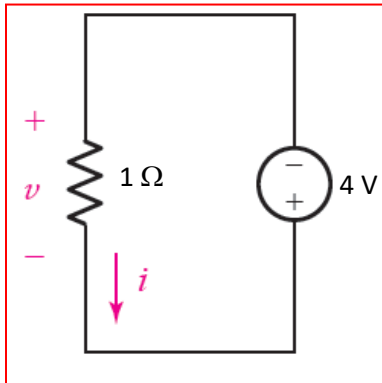

(all other sources are irrelevant to determining  $i$  and  $v$ ).

42. Left-hand network:  $1 + 2 \parallel 2 = 1 + 1 = 2 \Omega$

Right-hand network:  $4 + 1 \parallel (2 + 3) = 4 + 0.6667 + 3 = 7.667 \Omega$

43. For Fig. 3.82(a),  $R_{eq} = 1 + 2 \parallel R = 1 + 2R/(R + 2)$

(a)  $R = 2 \Omega$  so  $R_{eq} = 2 \Omega$

(b)  $R = 4 \Omega$  so  $R_{eq} = 2.33 \Omega$

(c)  $R = 0 \Omega$  so  $R_{eq} = 1 \Omega$

For Fig. 3.82(b),  $1/R_{eq} = 1 + 1/R + 1/3$

(a)  $R = 2 \Omega$  so  $R_{eq} = 0.545 \Omega$

(b)  $R = 4 \Omega$  so  $R_{eq} = 0.632 \Omega$

(c)  $R = 0 \Omega$  so  $R_{eq} = 0.750 \Omega$

44. (a) The 4 resistors may be replaced with a single resistor having value

$$2 + 7 + 5 + 1 = 15 \Omega.$$


$$(b) I = (3 - 1) / 15 = 133.3 \text{ mA}$$

$$(c) 3 \text{ V}$$

$$(d) P_{1\Omega} = i^2 R = 17.78 \text{ mW}$$

45. KCL yields  $i_{eq} = -2 + 5 + 1 = 4 \text{ A}$   
And  $R_{eq} = 5 \parallel 5 = 2.5 \Omega$

(a)

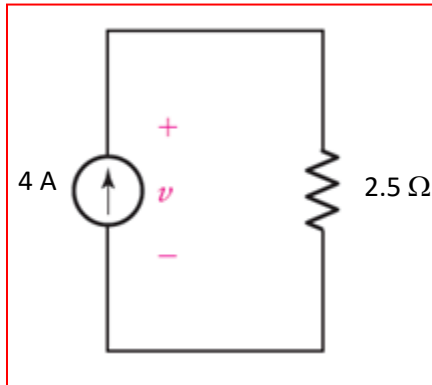

(b) Ohm's law yields  $v = (4)(2.5) = 10 \text{ V}$

(c) Power *supplied* by 2 A source =  $(-2)(10) = -20 \text{ W}$

46. We can create an effective resistance by making the following combination to appear in parallel with the 1 A source:

$$6 \parallel 3 + 1 + 5 + 3 \parallel 6 = 10 \Omega.$$

Noting that  $3 \parallel 10 \parallel 5 = 1.579 \Omega$ , we can compute  $v_x = (1)(1.579) = 1.579 \text{ V}$ .

Then,  $i_3 = v_x/3 = 536.3 \text{ mA}$


47. At the far right we have the resistor combination  $9 + 6 \parallel 6 = 9 + 3 = 12 \Omega$ .  
 After this, we have three resistors in parallel but should not involve the  $15 \Omega$  resistor as it controls the dependent source. Thus,  $R_{eq}^{-1} = 1/3 + 1/12$  and  $R_{eq} = 2.4 \Omega$ .  
 The simplified circuit is shown below.  
 Summing the currents flowing into the top node,

$$2 - \frac{v_x}{2.4} - \frac{v_x}{15} - 4i = 0 \quad [1]$$

Since  $i = v_x/15$ , Eq. [1] becomes

$$2 - \frac{v_x}{2.4} - \frac{v_x}{15} - \frac{4}{15}v_x = 0$$

Solving,  $v_x = 2.667 \text{ V}$

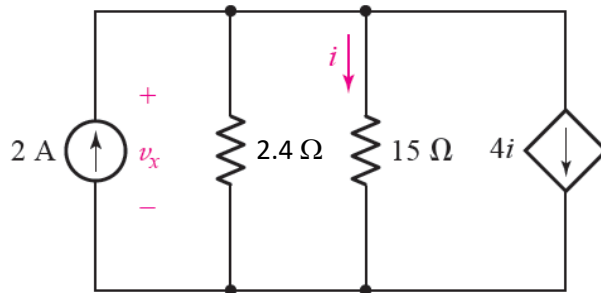

48. We combine the left-hand set of resistors:  $6 + 3 \parallel 15 = 8.5 \Omega$   
The independent sources may be combined into a single  $4 + 3 - 9 = -2$  A source (arrow pointing up). We leave the  $6 \Omega$  resistors; at least one has to remain as it controls the dependent source. A voltage  $v$  is defined across the simplified circuit, with the + terminal at the top node.

Applying KCL to the top node,

$$-2 - 2i = v/8.5 + v/6 + v/6 \quad [1]$$

where  $i = v/6$ . Thus, Eq. [1] becomes  $-2 - 2v/6 = v/8.5 + 2v/6$  or  $v = -2.55$  V.

We have lost the  $15 \Omega$  resistor temporarily, however. Fortunately, the voltage we just found appears across the original resistor combination we replaced. Hence, a current  $-2.55/8.5 = -0.3$  A flows downward through the combination.

Hence, the voltage across the  $3 \Omega \parallel 15 \Omega$  combination is

$$v - 6(-0.3) = -0.75 \text{ V}$$

$$\text{Thus, } P_{15\Omega} = (-0.75)^2/15 = \boxed{37.5 \text{ mW}}$$

49. Starting from the far right, we define  $R_A = R_7 \parallel [R_8 + R_{10} \parallel R_{11} + R_9]$   
 $= 10 \parallel [10 + 10 \parallel 10 + 10] = 10 \parallel 25 = 7.143 \Omega.$

Next,  $R_4 \parallel [R_5 + R_A + R_6] = 10 \parallel [10 + 7.143 + 10] = 7.308 \Omega$

Finally,  $R_{eq} = R_1 \parallel [R_2 + 7.308 + R_3] = 7.32 \Omega$

50. Four 100  $\Omega$  resistors may be combined as:

$$(a) 25 \Omega = 100 \Omega \parallel 100 \Omega \parallel 100 \Omega \parallel 100 \Omega$$

$$(b) 60 \Omega = [(100 \Omega \parallel 100 \Omega) + 100 \Omega] \parallel 100 \Omega$$

$$(c) 40 \Omega = (100 \Omega + 100 \Omega) \parallel 100 \Omega \parallel 100 \Omega$$

51. (a)  $v_2 = v_1 - v_2 = 9.2 - 3 = 6.2 \text{ V}$

(b)  $v_1 = v - v_2 = 2 - 1 = 1 \text{ V}$

(c)  $v = v_1 + v_2 = 3 + 6 = 9 \text{ V}$

(d)  $v_1 = vR_1/(R_1 + R_2) = v_2R_2/(R_1 + R_2)$ .

Thus, setting  $v_1 = v_2$  and  $R_1 = R_2$ ,  $R_1/R_2 = 1$

(e)  $v_2 = vR_2/(R_1 + R_2) = vR_2/(2R_2 + R_2) = v/3 = 1.167 \text{ V}$

(f)  $v_1 = vR_1/(R_1 + R_2) = (1.8)(1)/(1 + 4.7) = 315.8 \text{ mV}$

52. (a)  $i_1 = i - i_2 = 8 - 1 = 7\text{A}$

(b)  $v = i(R_1 \parallel R_2) = i(50 \times 10^3) = 50\text{ V}$

(c)  $i_2 = iR_1/(R_1 + R_2) = (20 \times 10^{-3})(1/5) = 4\text{ mA}$

(d)  $i_1 = iR_2/(R_1 + R_2) = (10)(9)/18 = 5\text{A}$

(e)  $i_2 = iR_1/(R_1 + R_2) = (10)(10 \times 10^6)/(10 \times 10^6 + 1) = 10\text{ A}$

53. **One** possible solution: Choose  $v = 2\text{ V}$  Then

$$R1 = v/i1 = 2\ \Omega$$

$$R2 = v/i2 = 1.67\ \Omega$$

$$R3 = v/i3 = 250\ \text{m}\Omega$$

$$R4 = v/i4 = 645\ \text{m}\Omega$$

54. First, replace the  $2\ \Omega \parallel 10\ \Omega$  combination with  $1.66\ \Omega$ . Then

$$v_x = 3 \frac{2}{2+3+1.667} = \boxed{900\ \text{mV}}$$

55. Employing voltage division,

$$V_{3\Omega} = (9)(3)/(1 + 3 + 5 + 7 + 9) = 1.08 \text{ V}$$

$$V_{7\Omega} = (9)(7)/(1 + 3 + 5 + 7 + 9) = 2.52 \text{ V}$$

56. We begin by simplifying the circuit to determine  $i_1$  and  $i_2$ .

We note the resistor combination  $(4 + 4) \parallel 4 + 5 = 8 \parallel 4 + 5 = 7.667 \Omega$ .

This appears in parallel with the  $1 \Omega$  and  $2 \Omega$  resistors, and experiences current  $i_2$ .

Define the voltage  $v$  across the  $25 \text{ A}$  source with the '+' reference on top. Then,

$$25 = \frac{v}{1} + \frac{v}{2} + \frac{v}{7.667}$$

Solving,  $v = 15.33 \text{ V}$ . Thus,  $i_1 = 25 - v/1 = 9.67 \text{ A}$

$$i_2 = i_1 - v/2 = 2.005 \text{ A}$$

Now, from current division we know  $i_2$  is split between the  $4 \Omega$  and  $4 \Omega + 4 \Omega = 8 \Omega$  branches, so we may write

$$v_3 = 4[4i_2/(4 + 8)] = \boxed{2.673 \text{ V}}$$

57. We may do a little resistor combining:

$$2 \text{ k}\Omega \parallel 4 \text{ k}\Omega = 8/6 \text{ k}\Omega$$

$$3 \text{ k}\Omega \parallel 7 \text{ k}\Omega = 21/10 \text{ k}\Omega$$

The  $4 \text{ k}\Omega$  resistor is in parallel with the series combination of  $8/6 + 3 + 21/10 = 6.433 \text{ k}\Omega$ . That parallel combination is equivalent to  $2.466 \text{ k}\Omega$ .

Thus, voltage division may be applied to yield

$$v_{4\text{k}\Omega} = (3)(2.466)/(1 + 2.466) = 2.134 \text{ V}$$

$$\text{and } v_x = (2.134)(21/10)/(8/6 + 3 + 21/10) = \boxed{697.0 \text{ mV}}$$

58. We *could* use voltage division for determining those voltages if  $i_B = 0$ . Since it is *nonzero* (presumably – circuit analysis will verify whether this is the case), we do not have equal currents through the two resistors, hence voltage division is not valid.

59. (a)  $i_{1k\Omega} = (-g_m v_\pi)(10/11)$  where  $v_\pi = 12 \times 10^{-3} (15/18) \cos 1000t$

Thus,  $i_{1k\Omega} = -10.9 \cos 1000t \mu\text{V}$

(b)  $v_{\text{out}} = (1 \times 10^3) i_{1k\Omega} = -10.9 \cos 1000t \text{ mV}$

(c)  $|v_{\text{out}}|/|v_s| = 10.9/12 < 1$ , so no, it does not amplify (in terms of voltage magnitude).

(d)  $|v_{\text{out}}|/|v_\pi| = 10.9/10 > 1$ , so yes.

60.  $v_{\text{out}} = (3.3 \times 10^3)(-g_m v_\pi) = (3.3 \times 10^3)(-322 \times 10^{-3})v_\pi$

where  $v_\pi = [6 \times 10^{-6} \cos 2300t] (45/18)/(1 + 45/18) = 4.286 \times 10^{-6} \cos 2300t \text{ V}$ .

Thus,  $v_{\text{out}} = 4.55 \cos 2300t \text{ mV}$

61. (a) Looking to the right of the  $10\ \Omega$  resistors, we see

$$40 + 50 \parallel (20 + 47) = 68.63\ \Omega$$

Further, the  $10\ \Omega \parallel 10\ \Omega$  can be replaced with a  $5\ \Omega$  resistor without losing the desired voltage. Hence,  $v$  appears across  $5 \parallel 68.63 = 4.66\ \Omega$

$$\text{So } v = 20(4.66)/(20 + 4.66) = \boxed{3.78\ \text{V}}$$

(b) The  $4\ \Omega$  resistor has been “lost” but we can return to the original circuit and note the voltage determined in the previous part. By voltage division, the voltage across the  $50\ \Omega$  resistor is  $v(50 \parallel 67)/(40 + 50 \parallel 67) = 1.57\ \text{V}$ .

$$v_{47\Omega} = v_{50\Omega}(47)/(20 + 47) = 1.10\ \text{V}$$

Hence, the power dissipated by the  $47\ \Omega$  resistor is  $(v_{47\Omega})^2/4 = \boxed{25.7\ \text{mW}}$

(d)  No, the power consumption (26 mW) is far below the maximum rating of 250 mW.

62. (a) Define

$$R_{\text{eq}} = 40 + 50 \parallel (20 + 47) = 68.63 \Omega$$

$$R_{\text{TOTAL}} = 20 + 10 \parallel R_{\text{eq}} = 28.73 \Omega$$

$$i_{\text{total}} = 20/R_{\text{TOTAL}} = 0.696 \text{ A}$$

By current division,  $i_{40} = i_{\text{total}} (10/(10 + R_{\text{eq}})) = 8.5 \text{ mA}$

(b)  $P_{20\text{V}} = (20)i_{\text{total}} = (20)(0.696) = 13.92 \text{ W}$

(d)  $I_{50} = i_{40} (20 + 47)/[50 + (20 + 47)] = 0.0507 \text{ A}$

$$P_{50} = (i_{50})^2 \times 50 = 128 \text{ mW}$$

63. (a) 5 nodes; 6 loops; 7 branches;

(b) Define all currents as flowing either left to right or downward.

Note the combination  $R_{eq} = 2/3 + 2 + 5 = 7.667 \Omega$ .

By inspection,  $I_{2\Omega\text{left}} = -2 \text{ A};$

$$I_{5\Omega(\text{left})} = (-2)(7.667)/(5 + 7.667) = -1.21 \text{ A};$$

$$I_{2\Omega\text{right}} = I_{5\Omega} = (-2)(5)/(5 + 7.667) = -790 \text{ mA};$$

The remaining currents are found by current division:

$$I_{1\Omega} = -0.7895(2)/3 = -526 \text{ mA};$$

$$I_{2\Omega\text{middle}} = -0.7895(1)/3 = -263 \text{ mA}$$

$$(a) V_{2A} = V_{2\Omega(\text{left})} + V_{5\Omega(\text{left})} = (-2)(2) + (-1.211)(5) = -10.06 \text{ V}.$$