

1.

(a)  $5 \sin\left(5t - \frac{9\pi}{180}\right), t = 0, 0.01, 0.1 \text{ s}:$

 $-0.78; -0.53; 1.7$ 

(b)  $4 \cos 2t, t = 0, 1, 1.5 \text{ s}:$

 $4.0, -1.7, -4.0$ 

(c)  $3.2 \cos\left(6t + \frac{15\pi}{180}\right), t = 0, 0.01, 0.1:$

 $3.1, 3.0, 2.1$

2. (a)

$$300 \sin 628t = 300 \cos(628t - 90^\circ);$$

$$4 \sin(3\pi t + 30^\circ) = 4 \cos(3\pi t + 30^\circ - 90^\circ) = 4 \cos(3\pi t - 60^\circ);$$

$$\begin{aligned} 14 \sin(50t - 5^\circ) - 10 \cos 50t &= -10 \cos 50t + 14 [\cos(-5^\circ) \sin 50t - \sin(-5^\circ) \cos 50t] \\ &= -10 \cos 50t + 13.95 \sin 50t + 1.22 \cos 50t = -8.78 \cos 50t + 13.95 \sin 50t \\ &= \sqrt{(8.78)^2 + (13.95)^2} \cos\left(50t + \tan^{-1} \frac{13.95}{8.78}\right) = 16.48 \cos(50t + 57.8^\circ) \end{aligned}$$

(b)

$$2 \cos(100t + 45^\circ) = 2 \sin(100t + 45^\circ + 90^\circ) = 2 \sin(100t + 135^\circ);$$

$$3 \cos 4000t = 3 \sin(4000t + 90^\circ);$$

$$5 \cos(2t - 90^\circ) + 10 \sin(2t) = 5 \cos(2t - 90^\circ) + 10 \cos(2t - 90^\circ) = 15 \cos(2t - 90^\circ)$$

3.

$$v_1 = 10 \cos(10t - 45^\circ)$$

$$(a) i_1 = 5 \cos 10t \quad \therefore v_1 \text{ leads } i_1 \text{ by } -45^\circ$$

$$(b) i_1 = 5 \cos(10t - 80^\circ) \quad \therefore v_1 \text{ leads } i_1 \text{ by } -45 - (-80) = +35^\circ$$

$$(c) i_1 = 5 \cos(10t - 40^\circ) \quad \therefore v_1 \text{ leads } i_1 \text{ by } -45 - (-40) = -5^\circ$$

$$(d) i_1 = 5 \cos(10t + 40^\circ) \quad \therefore v_1 \text{ leads } i_1 \text{ by } -45 - 40 = -85^\circ$$

$$(e) i_1 = 5 \cos(10t - 19^\circ) \quad \therefore v_1 \text{ leads } i_1 \text{ by } -45 - (-19) = -26^\circ$$

4.

$$v_1 = 3 \cos(10^4 t - 5^\circ) \text{ lags}$$

$$(a) 5 \cos 10^4 t \text{ by } 0 - (-5) = \boxed{+5^\circ}$$

$$(b) 5 \cos(10^4 t - 14^\circ) \text{ by } -14 - (-5) = \boxed{-9^\circ}$$

$$(c) 5 \cos(10^4 t - 23^\circ) \text{ by } -23 - (-5) = \boxed{-18^\circ}$$

$$(d) 5 \cos(10^4 t + 23^\circ) \text{ by } 23 - (-5) = \boxed{28^\circ}$$

$$(e) \sin(10^4 t - 390^\circ) = 5 \cos(10^4 t - 30^\circ - 90^\circ) \text{ by } -120 - (-5) = \boxed{-115^\circ}$$

5. (a)  $\cos 4t = \sin(4t + 90^\circ)$  so  $\sin 4t$  lags  $\cos 4t$  (by  $90^\circ$ )

(b)  $\cos(4t - 80^\circ)$  lags  $\cos 4t$  (by  $80^\circ$ )

(c)  $\cos 4t$  lags  $\cos(4t + 80^\circ)$  (by  $80^\circ$ )

(d)  $-5 \sin 5t = 5 \sin(5t + 180^\circ) = 5 \cos(5t + 90^\circ)$

so

$\cos(5t + 2^\circ)$  lags  $-5 \sin 5t$  (by  $90 - 2 = 88^\circ$ )

(e)  $\sin 5t + \cos 5t = \sqrt{2} \cos(5t + \tan^{-1}(-1)) = \sqrt{2} \cos(5t - 45^\circ)$   
 which neither leads nor lags  $\cos(5t - 45^\circ)$ !

6. (a)

$$\cos 3t - 7 \sin 3t = \sqrt{1+49} \cos(3t + \tan^{-1} 7) = 7.07 \cos(3t + 81.9^\circ)$$

$$= 0 \text{ at } 3t + 81.9^\circ = 3t + \frac{81.9\pi}{180} = \frac{\pi}{2}n, n = 1, 3, 5, \dots$$

$$\text{or } t = 0.0471 \text{ s, } 1.09 \text{ s, and } 6.42 \text{ s}$$

(b) already a single sinusoid so zero at  $10t + 45^\circ = 10t + \frac{45\pi}{180} = \frac{\pi}{2}n, n = 1, 3, 5, \dots$

$$\text{or } t = 0.0785 \text{ s, } 0.393 \text{ s, and } 0.707 \text{ s}$$

(c)

$$\cos 5t - \sin 5t = \sqrt{1+1} \cos(5t + \tan^{-1}(1)) = \sqrt{2} \cos(5t + 45^\circ)$$

$$= 0 \text{ at } 5t + \frac{45\pi}{180} = \frac{\pi}{2}n, n = 1, 3, 5$$

$$\text{or } t = 0.157 \text{ s, } 0.785 \text{ s, and } 1.41 \text{ s}$$

7.

(a)

$$\cos 3t - 7 \sin 3t = \sqrt{1+49} \cos(3t + \tan^{-1}(7)) = \sqrt{50} \cos(3t + 81.9^\circ)$$

$$= 1 \text{ at } \cos(3t + 81.9^\circ) = 0.1414$$

or

$$3t + \frac{81.9\pi}{180} = 1.429$$

Solving,  $t = -1.42 \times 10^{-4}$  s, which is not a valid solution.

Adding  $2\pi$ ,

$$3t = 1.429 + 2\pi - \frac{81.9\pi}{180}, \text{ or } t = 2.094 \text{ s}$$

Adding  $4\pi$ ,

$$3t = 1.429 + 4\pi - \frac{81.9\pi}{180}, \text{ or } t = 4.189 \text{ s}$$

$$\cos(10t + 45^\circ) = 1$$

or

$$10t = \cos^{-1}(1) - 45^\circ$$


Solving,  $t = -0.0785$  s, which is not a valid solution.

Adding  $2\pi$ ,

$$10t + 45^\circ = 0 + 2\pi, \text{ or } t = 0.5498 \text{ s}$$

Adding  $4\pi$ ,

$$t = 1.178 \text{ s}$$

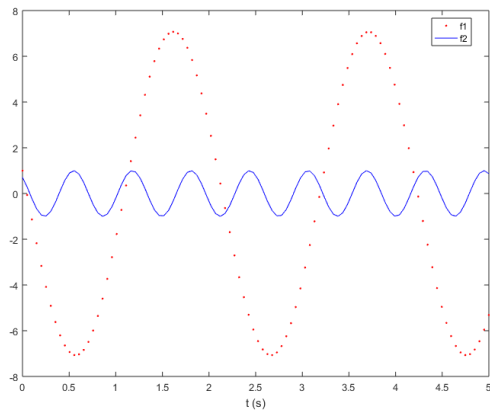

(b)

```
>> t = linspace(0,5,100);
>> f1 = cos(3*t)-7*sin(3*t);
>> f2 = cos(10*t+45*pi/180);
>> plot(t,f1,'r.',t,f2,'b-');legend;xlabel('t (s)');
f1 >> |
```

8. (a) (0,0); (0.5,1):  $v-0 = \frac{1-0}{0.5-0}(t-0)$  or  $v(t) = 2t$

Thus,  $v(0.25) = 2(0.25) = 0.50 \text{ V}$

(b)

$$v(t) \approx \frac{8}{\pi^2} \sin \pi t$$


so  $v(0.25) = \frac{8}{\pi^2} \sin 0.25\pi = 0.573 \text{ V}$

(c)

$$v(t) \approx \frac{8}{\pi^2} \left( \sin \pi t - \frac{1}{9} \sin 3\pi t + \frac{1}{25} \sin 5\pi t \right)$$

so  $v(0.25) = \frac{8}{\pi^2} \left( \sin 0.25\pi - \frac{1}{9} \sin 0.75\pi + \frac{1}{25} \sin 1.25\pi \right) = 0.487 \text{ V}$

(d,e,f)

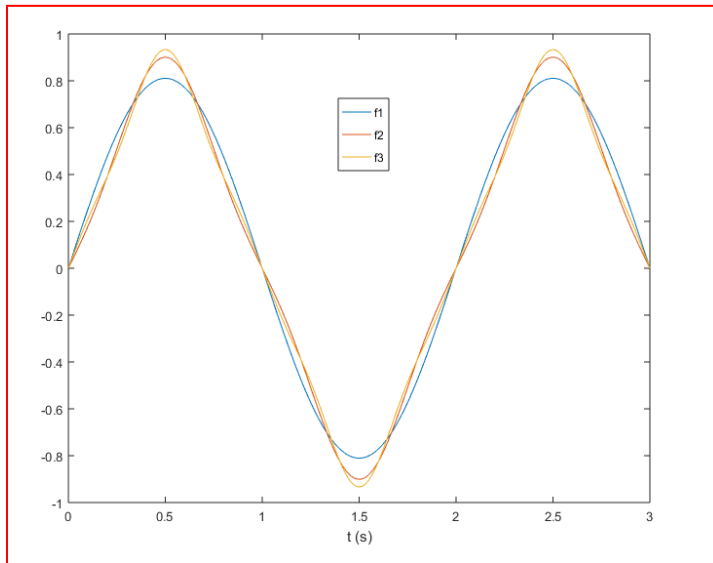

```
>> t = linspace(0,3,500);
>> f1 = (8/pi^2)*sin(pi*t);
>> f2 = (8/pi^2)*(sin(pi*t) - (1/9)*sin(3*pi*t));
>> f3 = (8/pi^2)*(sin(pi*t) - (1/9)*sin(3*pi*t) + (1/25)*sin(5*pi*t));
>> plot(t,f1,t,f2,t,f3);xlabel('t (s)');
fx >> |
```

9. (a)

$$V_{rms} = \left[ \frac{1}{T} \int_0^T V_m^2 \cos^2(\omega t) dt \right]^{\frac{1}{2}}$$

$$= \frac{V_m}{\sqrt{T}} \left[ \int_0^T V_m^2 \cos^2(\omega t) dt \right]^{\frac{1}{2}}$$

with  $u = \omega t$  and  $du = \omega dt$

$$V_{rms} = \frac{V_m}{\sqrt{T}} \left[ \int_0^{2\pi} \cos^2 u du \right]^{\frac{1}{2}} = \frac{V_m}{\sqrt{T}} \left[ \frac{T}{2\pi} \left( \frac{u}{2} + \frac{\sin 2u}{4} \right) \right]_0^{2\pi} = \frac{V_m}{\sqrt{T}} \left[ \frac{T}{2\pi} (2\pi + 0 - 0 - 0) \right]^{\frac{1}{2}}$$

$$= \frac{V_m}{\sqrt{2}}$$

(proof/derivation)

(b)  $110 V_{rms}$  corresponds to  $110\sqrt{2} = 156 \text{ V peak}$

$115 V_{rms}$  corresponds to  $115\sqrt{2} = 163 \text{ V peak}$

$120 V_{rms}$  corresponds to  $120\sqrt{2} = 170 \text{ V peak}$

10. Find the Thévenin equivalent by removing the inductor.

(a)

$$v_{TH} = \frac{1}{11} v_s = \frac{4.53}{11} \cos(30t) \text{ V}$$

$$R_{TH} = 10 \parallel 1 = \frac{10}{11} \Omega$$

From Eq.[4],

$$i_L(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos\left(\omega t - \tan^{-1} \frac{\omega L}{R}\right)$$

$$= \frac{\left(\frac{4.53}{11}\right)}{\sqrt{\left(\frac{10}{11}\right)^2 + 0.0081}} \cos\left(30t - \tan^{-1} \frac{(30)(0.003)}{10/11}\right)$$

$$= 0.451 \cos(30t - 5.65^\circ) \text{ A}$$

$$\text{So, } i_L(0) = 0.451 \cos(-5.65^\circ) = \boxed{0.449 \text{ A}}$$

(b)

$$v_L(t) = L \frac{di_L}{dt} = -(0.0003)(0.451)(30) \sin(30t - 5.65^\circ)$$

$$= -0.0406 \sin(30t - 5.65^\circ) \text{ V}$$

$$= 0.0406 \sin(30t + 174.35^\circ) \text{ V (if positive magnitude desired)}$$

11. Find the Thévenin equivalent after a quick source transformation. So,

$$V_{oc} = (25 \cos 100t)(1) \frac{2}{1+1+2} = 12.5 \cos 100t \text{ V and } R_{TH} = 1 \parallel 1 = 2 \Omega$$

From Eq. [4],

$$\begin{aligned} i_L(t) &= \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos\left(\omega t - \tan^{-1} \frac{\omega L}{R}\right) \\ &= \frac{12.5}{\sqrt{1+1}} \cos\left(100t - \tan^{-1} \frac{1}{1}\right) \end{aligned}$$

$$= 8.84 \cos(100t - 45^\circ) \text{ A}$$

12. Find the Thévenin equivalent after a quick source transformation. So,

$$V_{oc} = (25 \cos 100t)(1) \frac{2}{1+1+2} = 12.5 \cos 100t \text{ V and } R_{TH} = 1 \parallel 1 = 2 \Omega$$

From Eq. [4],

$$\begin{aligned} i_L(t) &= \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos\left(\omega t - \tan^{-1} \frac{\omega L}{R}\right) \\ &= \frac{12.5}{\sqrt{1+1}} \cos\left(100t - \tan^{-1} \frac{1}{1}\right) \end{aligned}$$

$$= 8.84 \cos(100t - 45^\circ) \text{ A}$$

$$\begin{aligned} v_L &= L \frac{di_L}{dt} = -10 \times 10^{-3} (8.84)(100) \sin(100t - 45^\circ) \\ &= -8.84 \sin(100t - 45^\circ) = 8.84 \sin(100t + 135^\circ) \text{ V} \end{aligned}$$

This is also the voltage across the  $2 \Omega$  resistor, so

$$\begin{aligned} P_{2\Omega} &= \frac{v_L^2}{2} = \frac{1}{2} (8.84)^2 \sin^2(100t + 135^\circ) \\ &= \boxed{39.1 \sin^2(100t + 135^\circ) \text{ W}} \end{aligned}$$

13.

$$3 \cos 4t = v_C + 5i_C$$

where

$$i_C = C \frac{dv_C}{dt}.$$

$$\text{Thus, } 3 \cos 4t = v_C + 10 \frac{dv_C}{dt}$$

$$\text{With } v_C(t) = V_1 \cos 4t + V_2 \sin 4t,$$

$$\frac{dv_C}{dt} = -4V_1 \sin 4t + 4V_2 \cos 4t$$

and so

$$V_1 \cos 4t + V_2 \sin 4t + 40V_2 \cos 4t - 40V_1 \sin 4t = 3 \cos 4t$$

We now can obtain two equations in our two unknowns:

$$V_1 + 40V_2 = 3 \quad [1]$$

$$-40V_1 + V_2 = 0 \quad [2]$$

Solving,

$$V_1 = 0.00187 \text{ V}$$

$$V_2 = 0.0750 \text{ V}$$

Thus,

$$v_C(t) = 0.00187 \cos 4t + 0.0750 \sin 4t = \sqrt{(0.00187)^2 + (0.0750)^2} \cos \left( 4t + \tan^{-1} \frac{(-0.075)}{0.00187} \right)$$

$$= 0.075 \cos(4t - 88.6^\circ) \text{ V}$$

14.

$$3 \cos 4t = v_C + 5i_C$$

where

$$i_C = C \frac{dv_C}{dt}$$

$$\text{Thus, } 3 \cos 4t = v_C + 10 \frac{dv_C}{dt}$$

$$\text{With } v_C(t) = V_1 \cos 4t + V_2 \sin 4t,$$

$$\frac{dv_C}{dt} = -4V_1 \sin 4t + 4V_2 \cos 4t$$

and so

$$V_1 \cos 4t + V_2 \sin 4t + 40V_2 \cos 4t - 40V_1 \sin 4t = 3 \cos 4t$$

We now can obtain two equations in our two unknowns:

$$V_1 + 40V_2 = 3 \quad [1]$$

$$-40V_1 + V_2 = 0 \quad [2]$$

Solving,

$$V_1 = 0.00187 \text{ V}$$

$$V_2 = 0.0750 \text{ V}$$

Thus,

$$\begin{aligned} v_C(t) &= 0.00187 \cos 4t + 0.0750 \sin 4t = \sqrt{(0.00187)^2 + (0.0750)^2} \cos \left( 4t + \tan^{-1} \frac{(-0.075)}{0.00187} \right) \\ &= 0.075 \cos(4t - 88.6^\circ) \text{ V} \end{aligned}$$

Since

$$\begin{aligned} w_C(t) &= \frac{1}{2} C v_C^2 = \left(\frac{1}{2}\right)(2) [0.075 \cos(4t - 88.6^\circ)]^2 \\ &= 0.0563 \cos^2(4t - 88.6^\circ) \text{ J} \end{aligned}$$

$$\text{At } t = 0.785 \text{ s, } w_C = 2.94 \text{ } \mu\text{J}$$

and

$$\text{At } t = 1.57 \text{ s, } w_C = 2.54 \text{ } \mu\text{J}$$

15. KCL yields

$$\cos 6t + 0.2i_L = i_L + \frac{v_L}{10}$$

where

$$v_L = L \frac{di_L}{dt}$$

so

$$\cos 6t = 0.8i_L + 0.5 \frac{di_L}{dt} \quad [1]$$

$$i_L(t) = I_1 \cos 6t + I_2 \sin 6t$$

$$\frac{di_L}{dt} = -6I_1 \sin 6t + 6I_2 \cos 6t \quad [2]$$

Substituting Eq [2] into Eq [1],

$$\cos 6t = 0.8I_1 \cos 6t + 0.8I_2 \sin 6t + 3I_2 \cos 6t - 3I_1 \sin 6t$$

We can use this to generate two equations in two unknowns:

$$0.8I_1 + 3I_2 = 1$$

$$-3I_1 + 0.8I_2 = 0$$

Solving,

$$I_1 = 0.083 \text{ A}$$

$$I_2 = 0.31 \text{ A}$$

Thus,

$$i_L(t) = 0.321 \cos(6t - 75^\circ) \text{ A}$$

Then,

$$v_L = L \frac{di_L}{dt} = -(0.5)(0.321)(6) \sin(6t - 75^\circ)$$

$$= -0.963 \sin(6t - 75^\circ) = 0.963 \sin(6t + 105^\circ) \text{ V} = v_R$$

Hence,

$$P_R = \frac{1}{10} v_L^2 = 0.0927 \sin^2(6t + 105^\circ) \text{ W}$$

16.

$$(a) 50 \cos(-75^\circ) + j \sin(-75^\circ) = 12.94 - j48.30$$

$$(b) 19 \angle 30^\circ = 16.45 + j9.5$$

$$(c) 2.5 \angle -30^\circ + 0.5 \angle 45^\circ = 2.52 - j0.896$$

$$(d) (2 + j2)(2 - j2) = 8 + j0 = 8 \angle 0$$

$$(e) (2 + j2)(5 \angle 22^\circ) = (2.83 \angle 45^\circ)(5 \angle 22^\circ) = 14.15 \angle 67^\circ$$

17. (a)  $1 + e^{j45^\circ} = 1 + 1\angle 45^\circ = 1 + 0.707 + j0.707 = 1.85\angle 22.5^\circ$

(b)  $-j(j)^2 = +j = 1\angle 90^\circ$

(c)  $32 = 32\angle 0^\circ$

(d)  $2 - e^{j45^\circ} = 2 - 1\angle 45^\circ = 2 - 0.707 - j0.707 = 1.293 - j0.707$

(f)  $-j + 5\angle 0 = -j + 5 = 5 - j$

18. (a)  $4(8 - j8) = (4\angle 0)(11.31\angle -45^\circ) = 43.25\angle -45^\circ$

(b)  $4\angle 5^\circ - 2\angle 15^\circ = 3.98 + j0.349 - 1.93 - j0.518 = 2.06\angle -4.71^\circ$

(c)  $2 + j9 - 5\angle 0 = 2 + j9 - 5 = -3 + j9 = 9.49\angle 108^\circ$

(d)

$$\begin{aligned} \frac{-j}{10 + j5} - 3\angle 40^\circ + 2 &= \frac{-j(10 - j5)}{(10 + j5)(10 - j5)} - 3\angle 40^\circ + 2 \\ &= 0.04 - j0.08 - 2.30 - j1.93 + 2 = 2.04\angle -99.6^\circ \end{aligned}$$

19. (a)  $3(3\angle 30^\circ) = 9\angle 30^\circ = 7.79 + j4.5$

(b)  $2\angle 25^\circ + 5\angle -10^\circ = 1.81 + j0.845 + 4.92 - j0.868 = 6.73 - j0.023$

(c)  $12 + j90 - 5\angle 30^\circ = 12 + j90 - 4.33 + j2.5 = 16.33 + j92.5$

(d)  $\frac{10 + j5}{8 - j} + 2\angle 60^\circ + 1 = 1.15 + j0.769 + 1 + j1.73 + 1 = 3.15 + j2.5$

20. (a)

$$\begin{aligned} \frac{2+j3}{1.8\angle 90^\circ} - 4 &= \frac{3.61\angle 56.3^\circ}{1.8\angle 90^\circ} - 4 = 2.01\angle 26.3^\circ - 4 \\ &= 1.798 + j0.889 - 4 = \boxed{2.37\angle 158^\circ} \end{aligned}$$

$$\frac{10\angle 25^\circ}{5\angle -10^\circ} + \frac{3\angle 15^\circ}{3-j5} = 2\angle 35^\circ + 0.514\angle 74^\circ$$

$$\begin{aligned} \text{(b)} &= 1.64 + j1.15 + 0.142 + j0.494 = 1.782 + j1.644 \\ &= \boxed{2.42\angle 42.7^\circ} \end{aligned}$$

$$\begin{aligned} \text{(c)} \quad &\frac{(1-j)(1+j)+1}{-j}(3\angle -90^\circ) + \frac{j}{1\angle -45^\circ} = \left( \frac{3\angle 0^\circ}{1\angle -90^\circ} \right) (3\angle -90^\circ) + \frac{1\angle 90^\circ}{1\angle -45^\circ} \\ &= 9\angle 0^\circ + 1\angle 138^\circ = 8.32\angle 4.87^\circ = \boxed{8.29 + j0.707} \end{aligned}$$

21.

$$5 \sin 20t \text{ V} \rightarrow 5e^{j20t} \text{ V}$$

$$KVL: -5e^{j20t} + 5i_C + v_C = 0$$

$$\text{where } i_C = C \frac{dv_C}{dt} = 0.13 \frac{dv_C}{dt}.$$

Thus,

$$5(0.13) \frac{dv_C}{dt} + v_C = 5e^{j20t} \quad [1]$$

Substituting

$$v_C = V_m e^{j(20t+\phi)}$$

into Eq. [1],

$$5(0.13)V_m(j20)e^{j(20t+\phi)} + V_m e^{j(20t+\phi)} = 5e^{j20t}$$

$$(j13V_m + V_m)e^{j(20t+\phi)} = 5e^{j20t}$$

Solving for  $V_m$ ,

$$V_m \sqrt{1+13^2} = 5 \quad \text{or} \quad V_m = 0.383 \text{ V}$$

and

$$\phi + \tan^{-1} \frac{13}{1} = 0 \quad \therefore \phi = -85.6^\circ$$

$$v_C(t) = 0.383 \sin(20t - 85.6^\circ) \text{ V}$$

Thus, and

$$i_C = C \frac{dv_C}{dt} = (0.13)(0.383)(20) \cos(20t - 85.6^\circ) = 0.996 \cos(20t - 85.6^\circ) \text{ A}$$

$$22. \quad i_s = 2 \cos 5t \text{ A} \rightarrow 2e^{j5t} \text{ A}$$

$$v_L = 2(i_s - i_L) = L \frac{di_L}{dt}$$

so

$$4e^{j5t} - 2i_L - 0.4 \frac{di_L}{dt} = 0$$

Using

$$i_L(t) = I_m e^{j(5t+\phi)}$$

$$\frac{di_L}{dt} = j5I_m e^{j(5t+\phi)}$$

and substituting into our circuit equation,

$$2I_m e^{j(5t+\phi)} + j2I_m e^{j(5t+\phi)} = 4e^{j5t}$$

Next, we note that

$$I_m \sqrt{2^2 + 2^2} = 4, \text{ so } I_m = 1.41 \text{ A}$$

and

$$\phi + \tan^{-1}\left(\frac{2}{2}\right) = 0 \therefore \phi = -45^\circ$$

Finally, we may write

$$i_L(t) = 1.41 \cos(5t - 45^\circ) \text{ A}$$

23.  $i_L = 1.8e^{j(5t+26.6^\circ)}$ , so we may write:

$$2I_m e^{j(5t+\phi)} + j2I_m e^{j(5t+\phi)} = 1.8e^{j(5t+26.6^\circ)}$$

Note that

$$I_m \sqrt{2^2 + 2^2} = 1.8 \therefore I_m = 0.636 \text{ A}$$

$$\phi + \tan^{-1}\left(\frac{2}{2}\right) = 26.6^\circ, \text{ so } \phi = -18.4^\circ$$

Consequently,

$$i_L(t) = 0.636 \cos(5t - 18.4^\circ) \text{ A}$$

$$v_L(t) = L \frac{di_L}{dt} = 0.4(0.636)(5) \cos(5t - 18.4^\circ)$$

$$= 1.272 \cos(5t - 18.4^\circ) \text{ V}$$

and

$$i_s(t) = i_L(t) + \frac{v_L}{2} = 0.636 \cos(5t - 18.4^\circ) + 0.636 \cos(5t - 18.4^\circ)$$

$$= \boxed{1.272 \cos(5t - 18.4^\circ) \text{ A}}$$

24.

$$i_L = I_m e^{j(25t+\phi)}$$

$$5 \sin(35t - 10^\circ) \text{ A} \rightarrow 5e^{j(35t-10^\circ)} \text{ A}$$

$$i_L = 5e^{j(35t-10^\circ)} - i_C \quad [1]$$

where

$$i_C = C \frac{dv_C}{dt} = 0.01 \frac{dv_C}{dt}$$

$$v_C = 6i_L + v_L = 6i_L + 0.4 \frac{dv_C}{dt}$$

so

$$\frac{dv_C}{dt} = 6(j35)I_m e^{j(35t+\phi)} + 0.4(j35)e^{j(35t+\phi)}$$

and Eq. [1] becomes

$$\text{Note that } I_m e^{j(35t+\phi)} = 5e^{j(35t-10^\circ)} - j2.1I_m e^{j(35t+\phi)} + 4.9e^{j(35t+\phi)}$$

Thus,

$$5 = I_m \left[ (1-4.9)^2 + (2.1)^2 \right]^{\frac{1}{2}} \quad \text{or } I_m = 5 / 4.429 = 1.13 \text{ A}$$

and

$$-10^\circ = \phi + \tan^{-1} \left( \frac{2.1}{1-4.9} \right) \quad \text{or } \phi = -38.3^\circ$$

Finally,

$$i_L(t) = 1.13 \cos(35t + 18.3^\circ) \text{ A} = 1.13 \sin(35t - 162^\circ) \text{ A}$$

25. (a)  $28\angle 0$

(b)  $32\angle(-90^\circ - 90^\circ) = 32\angle -180^\circ$

(c)  $1\angle(45^\circ - 90^\circ) = 1\angle -45^\circ$

(d)

$$5 \cos 10t + 8 \cos(10t + 45^\circ) = 5 \cos 10t + 8[\cos 45^\circ \cos 10t - \sin 45^\circ \sin 10t]$$

$$= 5 \cos t + 4\sqrt{2} \cos 10t - 4\sqrt{2} \sin 10t = (5 + 4\sqrt{2}) \cos 10t - 4\sqrt{2} \sin 10t$$

$$= \sqrt{(5 + 4\sqrt{2})^2 + (4\sqrt{2})^2} \cos\left(10t + \tan^{-1} \frac{4\sqrt{2}}{5 + 4\sqrt{2}}\right)$$

$$= 12.1 \cos(10t + 28^\circ)$$

26. (a)  $11\angle -90^\circ$

(b)  $11\angle 0$

(c)  $11\angle -90^\circ$

(d)  $3\cos 100t - 3\sin 100t = A\cos\left(100t + \tan^{-1}\frac{3}{3}\right) = 4.24\cos(100t + 45^\circ)$

$$27. \quad \omega = 2\pi f = 2\pi(1000) = 6280 \text{ rad/s}$$

$$(a) \quad 9\angle 65^\circ \text{ V} \rightarrow 9\cos(6280t + 65^\circ) \text{ V}$$

$$(b) \quad \frac{2\angle 31^\circ}{4\angle 25^\circ} \text{ A} = 0.5\angle 6^\circ \rightarrow 0.5\cos(6280t + 6^\circ) \text{ A}$$

$$(c) \quad 22\angle 14^\circ - 8\angle 33^\circ \text{ V} = 21.35 + j5.32 - 6.71 - j4.36 = 14.64 - j0.96 \\ = 14.67\angle -3.75^\circ \text{ V} \\ \rightarrow 14.67\cos(6280t - 3.75^\circ) \text{ V}$$

$$28. \quad (a) \quad \frac{2-j}{5\angle 45^\circ} \text{ V} = \frac{2.24\angle -26.6^\circ}{5\angle 45^\circ} = 0.448\angle -71.6^\circ \text{ V}$$

$$(b) \quad \frac{6\angle 20^\circ}{1000} - j \text{ V} = 0.006\angle 20^\circ - j = 0.00564 + j0.00205 - j$$

$$= 0.00564 - j0.998 = 0.998\angle 89.7^\circ \text{ V}$$

$$(c) \quad (j)(52.5\angle -90^\circ) = (1\angle 90^\circ)(52.5\angle -90^\circ) = 52.5\angle 0^\circ \text{ V}$$

29.  $f = 50 \text{ Hz}$  so  $\omega = 2\pi f = 314 \text{ rad/s}$

(a)  $\frac{2-j}{5\angle 45^\circ} = \frac{2.24\angle -26.6^\circ}{5\angle 45^\circ} = 0.448\angle -71.6^\circ \text{ V}$

Thus,

$$v(t) = 0.448 \cos(314t - 71.6^\circ) \text{ V}$$

$$v(0.01) = -0.141 \text{ V}$$

$$v(0.025) = 0.426 \text{ V}$$

(b)  $\frac{2\angle 31^\circ}{4\angle 25^\circ} = 0.998\angle -89.7^\circ \text{ V}$

Thus,

$$v(t) = 0.998 \cos(314t - 89.7^\circ) \text{ V}$$

$$v(0.01) = -0.00364 \text{ V}$$

$$v(0.025) = 0.998 \text{ V}$$

(c)

$$(j)(52.5\angle -90^\circ) = 52.5\angle 0$$

so

$$v(t) = 52.5 \cos(314t + 0) = 52.5 \cos 314t \text{ V}$$

and

$$v(0.01) = -52.5 \text{ V}$$

$$v(0.025) = 0.209 \text{ V}$$

30.  $f = 50 \text{ Hz}$  so  $\omega = 2\pi f = 314 \text{ rad/s}$

(a)

$$v(t) = 9 \cos(314t + 65^\circ) \text{ V}$$

$\therefore$

$$v(0.01) = -3.82 \text{ V}$$

$$v(0.025) = -8.14 \text{ V}$$

(b)

$$i(t) = 0.5 \cos(314t + 6^\circ) \text{ A}$$

$\therefore$

$$i(0.01) = -0.497 \text{ A}$$

$$i(0.025) = -0.050 \text{ A}$$

(c)

$$v(t) = 14.67 \cos(314t - 3.75^\circ) \text{ V}$$

$$v(0.01) = -14.6 \text{ V}$$

$$v(0.025) = 1.02 \text{ V}$$

31.  $\omega = 5 \text{ rad/s}$ ;  $\mathbf{I} = 2\angle 0 \text{ mA}$

(a)  $\mathbf{V} = (1000)(0.002\angle 0) = 2\angle 0 \text{ V}$

(b)  $C = 0.001 \text{ F}$

$$\mathbf{V} = \frac{\mathbf{I}}{j\omega C} = \frac{0.002\angle 0}{j(5)(0.001)} = \frac{0.002\angle 0}{0.005\angle 90^\circ} = 0.4\angle -90^\circ \text{ V}$$

(c)  $L = 10^{-9} \text{ H}$

$$\mathbf{V} = j\omega L\mathbf{I} = j(5)(10^{-9})(0.002\angle 0) = 10^{-4}\angle 90^\circ \text{ V}$$

32.  $\omega = 1 \text{ rad/s}$

(a) If  $\mathbf{V}_R = 1\angle 30^\circ \text{ V}$ ,  $R = 1 \Omega$ , then  $\mathbf{I}_R = \mathbf{I}_C = \mathbf{I}_L = 1\angle 30^\circ \text{ A}$

(b)

$$\mathbf{V}_L = j\omega L \mathbf{I} = j(1)(1)\mathbf{I} = (1\angle 90^\circ)(1\angle 30^\circ) = 1\angle 120^\circ \text{ V}$$

$$\mathbf{V}_C = \frac{\mathbf{I}}{j\omega C} = \frac{1\angle 30^\circ}{j(1)(1)} = (1\angle 30^\circ)(1\angle -90^\circ) = 1\angle -60^\circ \text{ V}$$

$$\text{Ratio} = \frac{1\angle 30^\circ}{1\angle 120^\circ + 1\angle -60^\circ} = \frac{1\angle 30^\circ}{1.5\angle 119^\circ} = 0.667\angle -89^\circ$$

(c)

$$\omega = 2 \text{ rad/s} \therefore$$

$$\mathbf{V}_L = 2\angle 120^\circ \text{ V}$$

$$\mathbf{V}_C = 0.5\angle -60^\circ \text{ V}$$

$\therefore$

$$\text{Ratio} = \frac{1\angle 30^\circ}{2\angle 130^\circ + 0.5\angle -60^\circ} = \frac{1\angle 30^\circ}{0.51\angle 133^\circ} = 0.662\angle -103^\circ$$

33.  $\omega = 314 \text{ rad/s}$ .  $\mathbf{I} = 10\angle 0 \text{ mA} = 0.01\angle 0 \text{ A}$

(a)  $2 \Omega$ :  $\mathbf{V}_R = 2\mathbf{I} = 0.02\angle 0 \text{ V}$

(b)  $1 \text{ F}$ :  $\mathbf{V}_C = \frac{\mathbf{I}}{j\omega C} = \frac{0.01\angle 0}{j(314)(1)} = 3.18 \times 10^{-5} \angle -90^\circ \text{ V}$

(c)  $1 \text{ H}$ :  $\mathbf{V}_L = j\omega L\mathbf{I} = j(314)(1)(0.01\angle 0) = 3.14\angle 90^\circ \text{ V}$

(d)  $2 \Omega, 1 \text{ F}$ :

$$\mathbf{V}_R = 0.02\angle 0 \text{ V}$$

$$\mathbf{V}_C = 3.18 \times 10^{-5} \angle -90^\circ \text{ V}$$

$$\mathbf{V}_{TRC} = \mathbf{V}_R + \mathbf{V}_C = 0.02\angle -90^\circ \text{ V}$$

(e)  $2 \Omega, 1 \text{ H}$ :

$$\mathbf{V}_R = 0.02\angle 0 \text{ V}$$

$$\mathbf{V}_L = 3.14\angle 90^\circ \text{ V}$$

$$\mathbf{V}_{TRL} = \mathbf{V}_R + \mathbf{V}_C = 3.14\angle 90^\circ \text{ V}$$

(f)

$$v_R(0) = 0.02 \cos(0) = 0.02 \text{ V}$$

$$v_C(0) = 3.18 \times 10^{-5} \cos(-90^\circ) = 0 \text{ V}$$

$$v_L(0) = 3.14 \cos(90^\circ) = 0 \text{ V}$$

$$v_{TRC}(0) = 0.02 \cos(-0.09^\circ) = 0.02 \text{ V}$$

$$v_{TRL}(0) = 3.14 \cos(89.6^\circ) = 0.0219 \text{ V}$$

34.  $\mathbf{I}_{10} = 0.002\angle 42^\circ \text{ A}$   
 $\mathbf{I} = 0.00141\angle -3^\circ \text{ A}$

(a)

$$\mathbf{I}_{10} - \mathbf{I} = \mathbf{I}_{25\Omega} = 0.00141\angle 86.6^\circ \text{ A}$$

$$\mathbf{V}_{25\Omega} = 25\mathbf{I}_{25\Omega} = 0.0354\angle -3^\circ \text{ V}$$

$$\frac{\mathbf{V}_{25\Omega}}{\mathbf{I}_{25\Omega}} = \frac{0.0354\angle 86.6^\circ}{0.00141\angle -3^\circ} = 25.1\angle 89.8^\circ \Omega$$

Since the voltage leads the current by essentially  $90^\circ$ , it is likely an inductor.

$$j\omega L = 25.1\angle 90^\circ$$

$\therefore$

(b)  $\omega L = 25.1$

so

$$L = \frac{25.1}{\omega} = \frac{25.1}{1000} = 25.1 \text{ mH}$$

35.  $\mathbf{I}_{10} = 4\angle 35^\circ \text{ A}$ ;  $\mathbf{V} = 10\angle 35^\circ \text{ V}$ ;  $\mathbf{I} = 2\angle 35^\circ \text{ A}$

(a) No phase shift exists between  $\mathbf{I}_{10}$  and  $\mathbf{V}$ , so the element is likely a simple resistor:

$$R = \frac{\mathbf{V}}{\mathbf{I}_{10}} = \frac{10\angle 35^\circ}{4\angle 35^\circ} = \frac{10}{4} = 2.5 \Omega$$

(b)

$$\mathbf{I}_{25} = \mathbf{I}_{10} - \mathbf{I} = 4\angle 35^\circ - 2\angle 35^\circ = 2\angle 35^\circ \text{ A}$$



$$\mathbf{V}_{25} = 25(2\angle 35^\circ) = 50\angle 35^\circ \text{ V}$$

$$\begin{aligned} \mathbf{V}_s &= 10\mathbf{I}_{10} + \mathbf{V} + \mathbf{V}_{25} = 40\angle 35^\circ + 10\angle 35^\circ + 50\angle 35^\circ \\ &= 100\angle 35^\circ \text{ V} \end{aligned}$$

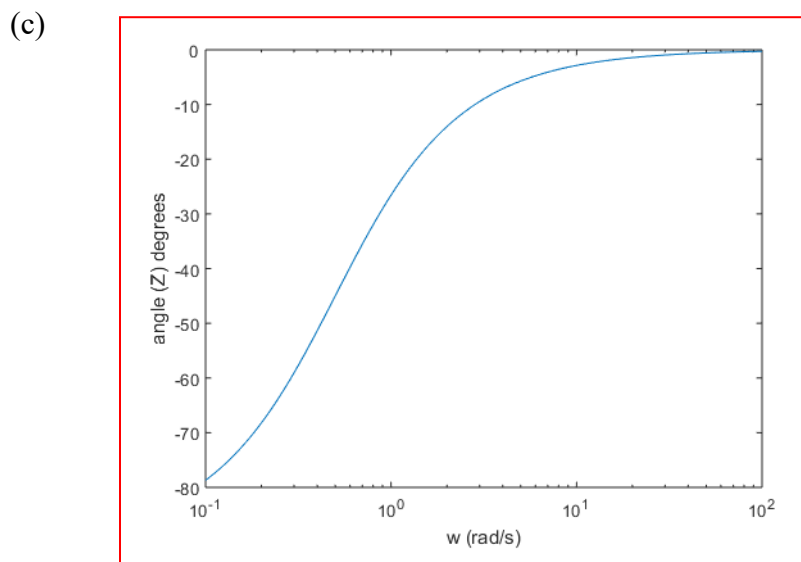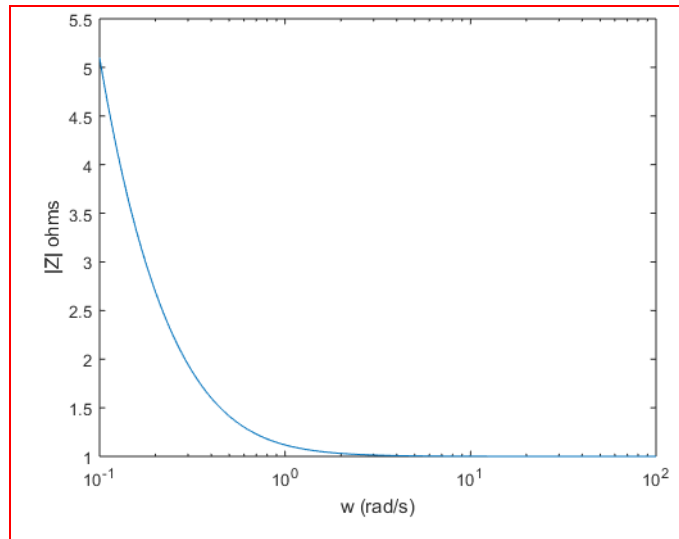36. (a)  $Z_{eq} = 1 + \frac{1}{j2\omega} \Omega$

(b) 

```
>> w=logspace(-1,2,500);  
Zeq = 1 + 0.5/i./w;  
Zmag=abs(Zeq);  
Zang=angle(Zeq)*180/pi;  
>> semilogx(w,Zang);xlabel('w (rad/s)');ylabel('angle (Z) degrees');
```



37.  $\omega = 20 \text{ rad/s}$

(a) We have  $1 \text{ k}\Omega \parallel 1 \text{ mH}$ :

$$\mathbf{Z}_R = 1000 \Omega$$

$$\mathbf{Z}_L = j\omega L = j(20)(10^{-3}) = j20 \times 10^{-3} \Omega$$

$$\mathbf{Z}_{\text{eff}} = \frac{(1000)(j20 \times 10^{-3})}{1000 + j20 \times 10^{-3}} = \boxed{0.02 \angle 90^\circ \Omega}$$

(b)

$$\mathbf{Z}_s = j\omega L + \frac{1}{j\omega C} = j(20)(1) + \frac{1}{j(20)(1)} = 19.5 \angle 90^\circ \Omega$$

$$\mathbf{Z}_{\text{eq}} = \frac{(10)(19.5 \angle 90^\circ)}{10 + 19.5 \angle 90^\circ} = \boxed{8.9 \angle 27^\circ \Omega}$$


38. (a)

$$\mathbf{Z}_L = j\omega L = j\omega(0.01)$$

$$\mathbf{Z}_{eq} = \frac{(1)(j\omega 0.01)}{1 + j0.01\omega} = \frac{j0.01\omega}{1 + j0.01\omega} \Omega$$

(b)
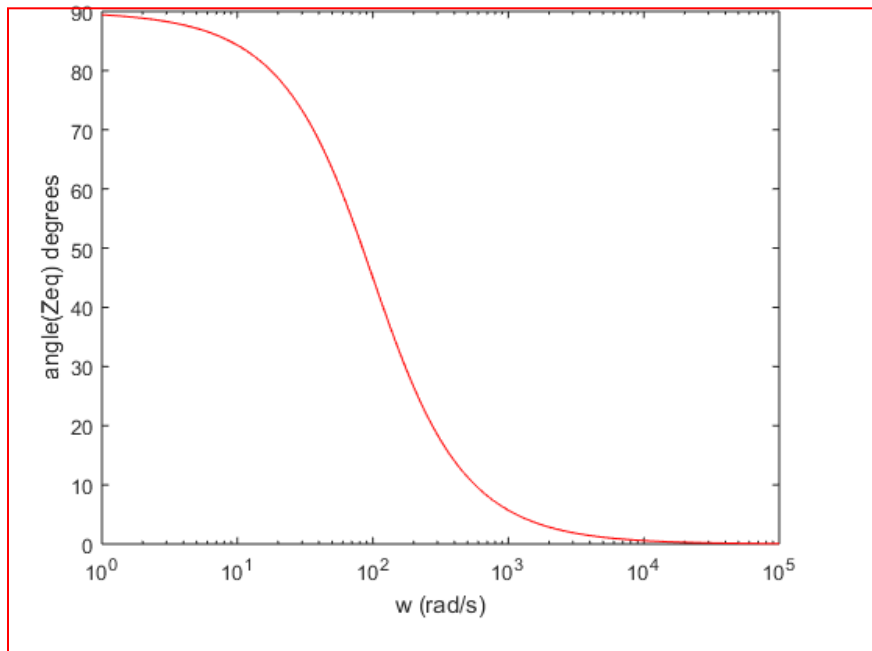
```
>> w=logspace(0,5,500);  
>> Zeq = i*0.01*w./(1+i*0.01*w);  
>> Zang=angle(Zeq)*180/pi;  
>> semilogx(w,Zang,'r-');xlabel('w (rad/s)');ylabel('angle(Zeq) degrees');
```



As a side note, as the angle of the effective impedance approaches zero, the impedance increasingly appears to be a simple resistance.

39.  $\omega = 1000 \text{ rad/s}$

(a)

$$\mathbf{Z}_L = j\omega L = j(1000)(0.02) = j0.02 \ \Omega$$

$$\mathbf{Z}_{eq} = 25 + \mathbf{Z}_L = 25 + j20 \ \Omega = 32 \angle 38.7^\circ \ \Omega$$

$$\mathbf{Y}_{eq} = \frac{1}{\mathbf{Z}_{eq}} = 0.031 \angle -39^\circ \text{ S}$$

(b)  $\mathbf{Y}_{eq} = \frac{1}{j20} + \frac{1}{25} = 0.064 \angle -51.3^\circ \text{ S}$

(c)  $\mathbf{Y}_{eq} = \frac{1}{j20} + \frac{1}{25} + j\omega C = 0.064 \angle -51.3^\circ \text{ S} + j(1000)(20 \times 10^{-3})$   
 $= 20 \angle 90^\circ \text{ S}$

40.

$$\mathbf{Z}_1 = 55 \parallel j\omega L = \frac{(55)(j0.02\omega)}{55 + j0.02\omega}$$

$$\mathbf{Z}_2 = \frac{1}{j\omega C} + 20 = 20 - \frac{j100}{\omega} = \frac{20\omega - j100}{\omega}$$

$$\mathbf{Z}_{eq} = 25 \parallel (\mathbf{Z}_1 + \mathbf{Z}_2)$$

(a)

$$\omega = 1 \text{ rad/s}$$

$$\mathbf{Z}_1 = 0.02 \angle 90^\circ \Omega$$

$$\mathbf{Z}_2 = 102 \angle -79^\circ \Omega$$

$$\mathbf{Z}_{eq} = \frac{(25)(0.02 \angle 90^\circ + 102 \angle -79^\circ)}{25 + 0.02 \angle 90^\circ + 102 \angle -79^\circ} = 23.3 \angle -13^\circ \Omega$$

(b)

$$\omega = 10 \text{ rad/s}$$

$$\mathbf{Z}_1 = 0.2 \angle 88^\circ \Omega$$

$$\mathbf{Z}_2 = 22.4 \angle -26.6^\circ \Omega$$

$$\mathbf{Z}_{eq} = \frac{(25)(0.2 \angle 88^\circ + 22.4 \angle -26.6^\circ)}{25 + 0.2 \angle 88^\circ + 22.4 \angle -26.6^\circ} = 12.1 \angle -13.8^\circ \Omega$$

(c)


$$\omega = 100 \text{ rad/s}$$

$$\mathbf{Z}_1 = 2 \angle 88^\circ \Omega$$

$$\mathbf{Z}_2 = 20 \angle -3^\circ \Omega$$

$$\mathbf{Z}_{eq} = \frac{(25)(2 \angle 88^\circ + 20 \angle -3^\circ)}{25 + 2 \angle 88^\circ + 20 \angle -3^\circ} = 11.1 \angle 1.5^\circ \Omega$$

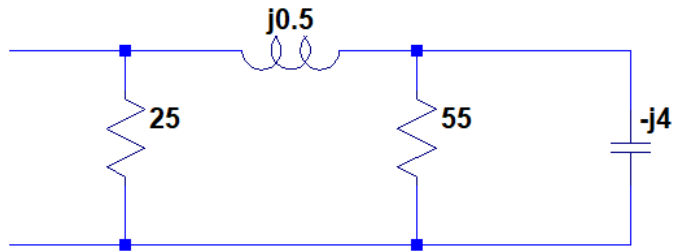41. Redrawing as directed, we obtain (all quantities shown in ohms):



$$j\omega L = j(25)(0.02) = j0.5 \Omega$$

$$\frac{1}{j\omega C} = \frac{1}{j(250)(0.01)} = -j4 \Omega$$

$$\mathbf{Z}_1 = 55 \parallel (-j4) = 4 \angle -86^\circ \Omega$$

$$\mathbf{Z}_2 = 20 + j0.5 = 20 \angle 1.4^\circ \Omega$$

$$\mathbf{Z}_{eq} = 25 \parallel (\mathbf{Z}_1 + \mathbf{Z}_2) = 25 \parallel \angle -10^\circ \Omega$$

Thus,

$$\mathbf{Z}_{eq} = 25 \parallel \angle -5.5^\circ \Omega$$

42.  $\mathbf{I} = 3\angle -20^\circ \text{ A}$ ,  $\omega = 2000 \text{ rad/s}$

(a)

$$\mathbf{Z} = 3 + j\omega L = 3 + j(2000)(0.002) = 3 + j4 \ \Omega$$

$$\mathbf{V} = \mathbf{Z} \cdot \mathbf{I} = (3\angle -20^\circ)(3 + j4) = (3\angle -20^\circ)(5\angle 53^\circ) = 15\angle 33^\circ \ \Omega$$

(b)

$$\mathbf{Z} = 3 - \frac{j}{\omega C} = 3 - \frac{j}{(2000)(125 \times 10^{-6})} = 5\angle -53^\circ \ \Omega$$

$$\mathbf{V} = \mathbf{Z} \cdot \mathbf{I} = (5\angle -53^\circ)(3\angle -20^\circ) = 15\angle -73^\circ \ \text{V}$$

(c)

$$\mathbf{Z} = 3 + j\omega L + \frac{1}{j\omega C} = 3 + 3 + j4 + 4\angle 90^\circ = 10\angle 53^\circ \ \Omega$$

$$\mathbf{V} = \mathbf{Z} \cdot \mathbf{I} = (3\angle -20^\circ)(10\angle 53^\circ) = 30\angle 33^\circ \ \text{V}$$

(d)  $\omega = 4000 \text{ rad/s}$

$$\mathbf{Z}_R = 3 \ \Omega$$

$$\mathbf{Z}_L = 3 + j(4000)(0.002) = 3 + j8 \ \Omega$$

$$\mathbf{Z}_C = \frac{-j}{(4000)(125 \times 10^{-6})} = 2\angle -90^\circ \ \Omega$$

$$\mathbf{Z} = \mathbf{Z}_R + \mathbf{Z}_L + \mathbf{Z}_C = 3 + 3 + j8 - j2 = 6 + j6 = 8.49\angle 45^\circ \ \Omega$$

$$\mathbf{V} = \mathbf{Z} \cdot \mathbf{I} = (3\angle -20^\circ)(8.49\angle 45^\circ) = 25.5\angle 25^\circ \ \text{V}$$

43.

$$\mathbf{Z}_1 = 60 \parallel \frac{-j}{\omega C} = 60 \parallel \left[ \frac{-j33.3 \times 10^{-3}}{\omega} \right] = (60) \left( \frac{\frac{-j33.3 \times 10^{-3}}{\omega}}{60 - \frac{j33.3 \times 10^{-3}}{\omega}} \right)$$

$$\mathbf{Z}_2 = 60 \parallel j\omega L = 60 \parallel [j\omega 0.01] = (60) \left( \frac{j\omega 0.01}{60 + j\omega 0.01} \right)$$

$$\mathbf{Z}_{eq} = 60 \parallel (\mathbf{Z}_1 + \mathbf{Z}_2)$$

(a)

$$f = 1 \text{ Hz} \rightarrow \omega = 2\pi f = 3.14 \text{ rad/s}$$

$$\mathbf{Z}_1 = 60 \angle -0.3^\circ \Omega$$

$$\mathbf{Z}_2 = 0.031 \angle 90^\circ \Omega$$

$$\mathbf{Z}_{eq} = \frac{60(60 \angle -0.3^\circ + 0.031 \angle 90^\circ)}{60 + 60 \angle -0.3^\circ + 0.031 \angle 90^\circ} \Omega = 30 \angle -0.15^\circ \Omega$$

(b)

$$\omega = 2\pi f = 6280 \text{ rad/s}$$

$$\mathbf{Z}_1 = 5.28 \angle -85^\circ \Omega$$

$$\mathbf{Z}_2 = 43.4 \angle 43.7^\circ \Omega$$

$$\mathbf{Z}_{eq} = \frac{60(5.28 \angle -85^\circ + 43.4 \angle 43.7^\circ)}{60 + 5.28 \angle -85^\circ + 43.4 \angle 43.7^\circ} \Omega = 25.4 \angle 22.8^\circ \Omega$$

(c)

$$\omega = 2\pi f = 6.28 \times 10^6 \text{ rad/s}$$

$$\mathbf{Z}_1 = 0.005 \angle -90^\circ \Omega$$

$$\mathbf{Z}_2 = 60 \angle 0.05^\circ \Omega$$

$$\mathbf{Z}_{eq} = \frac{60(0.005 \angle -90^\circ + 60 \angle 0.05^\circ)}{60 + 0.005 \angle -90^\circ + 60 \angle 0.05^\circ} \Omega = 30 \angle 0.02^\circ \Omega$$

(d)


$$\omega = 2\pi f = 6.28 \times 10^9 \text{ rad/s}$$

$$\mathbf{Z}_1 = 5.3 \times 10^{-6} \angle -90^\circ \Omega$$

$$\mathbf{Z}_2 = 60 \angle 0^\circ \Omega$$

$$\mathbf{Z}_{eq} = \frac{60(5.3 \times 10^{-6} \angle -90^\circ + 60 \angle 0^\circ)}{60 + 5.3 \times 10^{-6} \angle -90^\circ + 60 \angle 0^\circ} \Omega = 30 \angle 0^\circ \Omega$$

44. Drawing the circuit,

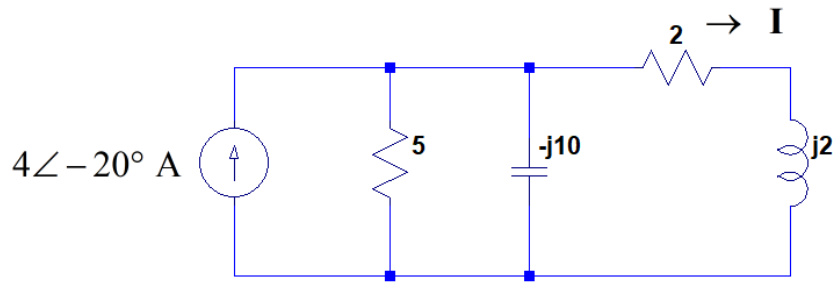

The current  $\mathbf{I}$  flows through the series combination  $2 + j2 \Omega$ . Thus, by current division,

$$\mathbf{I} = (4\angle -20^\circ) \frac{\frac{1}{2 + j2}}{5 - j10 + \frac{1}{2 + j2}} = (4\angle -20^\circ)(0.031\angle 17.9^\circ)$$

$$= 0.123\angle -2^\circ \text{ A}$$

Thus,

$$i(t) = 0.123 \cos(100t - 2^\circ) \text{ A}$$

45. **One possible set of solutions from many (design problem, so no unique solution):**  
Series combination of resistor (R), inductor (L), and capacitor (C).  $\omega = 100$  rad/s (given).

(a) **Set  $R = 1 \Omega$**

$$j\omega L - \frac{j}{\omega C} = 0$$

or

$$\text{Then, we need } \omega^2 = \frac{1}{LC} = (100)^2$$

$$\text{Setting } \mathbf{L = 1 \text{ mH,}}$$

$$\mathbf{C = 0.1 \text{ F}}$$

(b)

$$R + j\omega L - \frac{j}{\omega C} = 7 \angle 10^\circ = 6.89 + j1.22 \Omega$$

$$\left[ R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2 \right]^{\frac{1}{2}} = 7$$

or

$$R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2 = 49$$

Solving,

$$\left( \omega L - \frac{1}{\omega C} \right) = 1.22$$

$$\mathbf{\text{Set } L = 100 \text{ mH. Then } C = 1.14 \text{ mF and } R = 6.89 \Omega}$$

(c)

$$R + j\omega L - \frac{j}{\omega C} = 5 \angle -53.1^\circ = 3 - j4 = \Omega$$

$$\left[ R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2 \right]^{\frac{1}{2}} = 5$$

Solving,

$$\left( \omega L - \frac{1}{\omega C} \right) = -4$$

$$\mathbf{\text{Set } R = 3 \Omega \text{ and } L = 1 \text{ mH. Then } C = 2.44 \text{ mF.}}$$

46. **One possible set of solutions from many (design problem, so no unique solution):**  
Parallel combination of resistor (R), inductor (L), and capacitor (C).  $\omega = 10$  rad/s (given).

(a) We need

$$\mathbf{Y} = 1 \text{ S} = \frac{1}{R} + j\omega C - \frac{j}{\omega L}$$

$$\text{Setting } R = 1 \text{ } \Omega,$$

$$j\omega C - \frac{j}{\omega L} = 0$$

$$\text{or } \omega^2 = \frac{1}{LC}.$$

Set  $L = 1$  mH. Then,  $C = 10$  F.

This is not very realistic! Try  $C = 100$  mF. Then,  $L = 100$  mH.

(b)

$$\mathbf{Y} = 12 \angle -18^\circ \text{ S} = 11.41 - j3.71 \text{ S} = \frac{1}{R} + j\omega C - \frac{j}{\omega L}$$

$$\text{Setting } R = \frac{1}{11.41} = 0.0876 \text{ } \Omega,$$

$$j\omega C - \frac{j}{\omega L} = j \left( \omega C - \frac{1}{\omega L} \right) = -j3.71$$

$$\text{Set } C = 1 \text{ mF. Then, } L = 26.2 \text{ mH.}$$

(c)

$$\mathbf{Y} = 2 + j \text{ mS}$$


$$\text{Set } \frac{1}{R} = 0.002 \text{ S. } \therefore R = 500 \text{ } \Omega$$

Then

$$0.001j = j\omega C - \frac{1}{j\omega L}.$$

$$\text{Set } C = 100 \text{ mF. Then, } L = 100 \text{ mH}$$

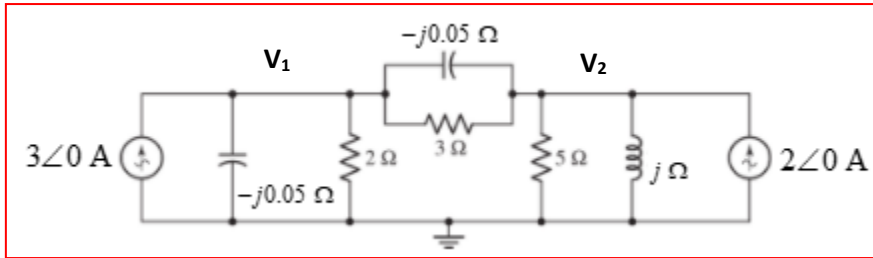47. (a) Redrawing the circuit in the phasor domain,



$$(b) \quad 3\angle 0 = \frac{V_1}{-j25} + \frac{V_1}{2} + \frac{V_1 - V_2}{-j0.05} + \frac{V_1 - V_2}{3} \quad [1]$$

$$2\angle 0 = \frac{V_2}{j} + \frac{V_2}{5} + \frac{V_2 - V_1}{3} + \frac{V_2 - V_1}{-j0.05} \quad [2]$$

Rearranging,

$$(j0.04 + 0.5 + j20 + 0.33)V_1 - (0.33 + j20)V_2 = 3 \quad [1]$$

$$-(0.33 + j20)V_1 + (-j + 0.2 + 0.33 + j20)V_2 = 2 \quad [2]$$

Solving,

$$V_1 = 4.11\angle 54.7^\circ \text{ V}$$


$$V_2 = 4.24\angle 54.5^\circ \text{ V}$$

Thus,

$$v_1(t) = 4.11 \cos(10t + 54.7^\circ) \text{ V}$$

$$v_2(t) = 4.24 \cos(10t + 54.5^\circ) \text{ V}$$

48. (a) Redrawing in the phasor domain,

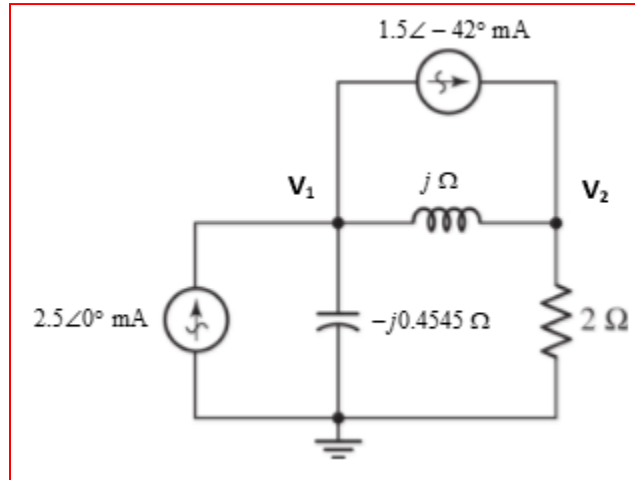

(b) We need only define one clockwise mesh current  $\mathbf{I}_3$  in the lower right mesh.

Then,

$$(-j0.4545)(\mathbf{I}_3 - 0.0025\angle 0) + j(\mathbf{I}_3 - 0.0015\angle -42^\circ) + 2\mathbf{I}_3 = 0$$

Solving,

$$\mathbf{I}_3 = \frac{-(+j0.4545)(0.0025) + (j)(0.0015\angle -42^\circ)}{-j0.454 + j + 2} = 4.28 \times 10^{-4} \angle -26^\circ \Omega$$

Thus,


$$i_1(t) = 2.5 \cos 10t \text{ mA} \quad \text{by inspection}$$

$$i_2(t) = 1.5 \cos(10t - 42^\circ) \text{ mA} \quad \text{by inspection}$$

and

$$i_3(t) = 0.43 \cos(10t - 26^\circ) \text{ mA}$$

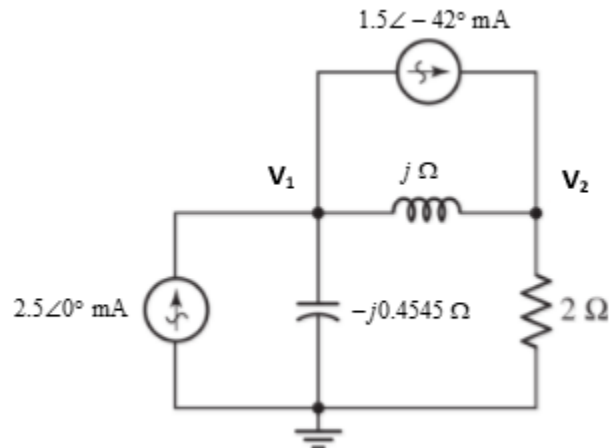49. We begin by redrawing in the phasor domain:



We require two nodal equations:

$$0.0025\angle 0 - 0.0015\angle -42^\circ = \frac{V_1}{-j0.4545} + \frac{V_1 - V_2}{j} \quad [1]$$

$$0.0015\angle -42^\circ = \frac{V_2}{2} + \frac{V_2 - V_1}{j} \quad [2]$$

Or

$$(j2.2 - j)V_1 + jV_2 = 0.00171\angle 35.9^\circ \quad [1]$$

$$jV_1 + (0.5 - j)V_2 = 0.0015\angle -42^\circ \quad [2]$$

Solving,

$$V_1 = 0.878\angle 32.7^\circ \text{ V}$$

$$V_2 = 1.05\angle -147^\circ \text{ V}$$

So,

$$v_1(t) = 0.878 \cos(10t + 32.7^\circ) \text{ V}$$

$$v_2(t) = 1.05 \cos(10t - 147^\circ) \text{ V}$$

50. By mesh analysis,

$$-10\angle -80^\circ + j30\mathbf{I}_1 + 55(\mathbf{I}_1 - \mathbf{I}_2) + 4\angle 0 = 0 \quad [1]$$

$$-4\angle 0 + 55(\mathbf{I}_2 - \mathbf{I}_1) - j20\mathbf{I}_2 + 2\angle -23^\circ = 0 \quad [2]$$

Grouping terms,

$$(55 + j30)\mathbf{I}_1 - 55\mathbf{I}_2 = 4 + 10\angle -80^\circ \quad [1]$$

$$-55\mathbf{I}_1 + (55 - j20)\mathbf{I}_2 = 4 - 2\angle -23^\circ \quad [2]$$

Solving,

$$\mathbf{I}_1 = 0.808\angle -111^\circ \text{ A}$$

$$\mathbf{I}_2 = 0.734\angle -89.1^\circ \text{ A}$$

51. By mesh analysis,

$$-3\angle 0 + j30\mathbf{I}_1 + 55(\mathbf{I}_1 - \mathbf{I}_2) + 5.5\angle -130^\circ = 0 \quad [1]$$

$$-5.5\angle -130^\circ + 55(\mathbf{I}_2 - \mathbf{I}_1) - j20\mathbf{I}_2 + 1.5\angle 17^\circ = 0 \quad [2]$$

Grouping terms,

$$(55 + j30)\mathbf{I}_1 - 55\mathbf{I}_2 = 7.78\angle 32.8^\circ \quad [1]$$

$$-55\mathbf{I}_1 + (55 - j20)\mathbf{I}_2 = 6.24\angle 142.8^\circ \quad [2]$$

Solving,

$$\mathbf{I}_1 = 0.433\angle 18.5^\circ \text{ A}$$

$$\mathbf{I}_2 = 0.358\angle 52.8^\circ \text{ A}$$

so

$$\frac{\mathbf{I}_1}{\mathbf{I}_2} = \frac{0.433\angle 18.5^\circ}{0.358\angle 52.8^\circ} = 1.21\angle -34.3^\circ$$

52. Begin by converting to phasor domain parameters:

$$2.5\angle 9^\circ \text{ V}$$

$$j10 \Omega$$

$$-j0.303 \Omega$$

Then, writing mesh equations:

$$-2.5\angle 9^\circ + 2\mathbf{I}_1 + j10(\mathbf{I}_1 - \mathbf{I}_2) = 0 \quad [1]$$

$$j10(\mathbf{I}_2 - \mathbf{I}_1) - j0.303\mathbf{I}_2 + 5\mathbf{I}_1 = 0 \quad [2]$$

Grouping terms,

$$(2 + j10)\mathbf{I}_1 - j10\mathbf{I}_2 = 2.5\angle 9^\circ \quad [1]$$

$$(5 - j10)\mathbf{I}_1 + j9.697\mathbf{I}_2 = 0 \quad [2]$$

Solving,

$$\mathbf{I}_1 = 0.349\angle 11.5^\circ \text{ A}$$

$$\mathbf{I}_2 = 0.402\angle 38.1^\circ \text{ A}$$

Thus,

$$i_1(t) = 0.349 \cos(10t + 11.5^\circ) \text{ A}$$

$$i_2(t) = 0.402 \cos(10t + 38.1^\circ) \text{ A}$$

53. By nodal analysis, we may write

$$-5\angle -18^\circ = \frac{\mathbf{V}_1}{j2} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{1 + j3.8} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{-j4} \quad [1]$$

$$2\angle 5^\circ = \frac{\mathbf{V}_2}{2} + \frac{\mathbf{V}_2 - \mathbf{V}_1}{-j4} + \frac{\mathbf{V}_2 - \mathbf{V}_1}{1 + j3.8} \quad [2]$$

Grouping terms,

$$\left[ \frac{1}{j2} + \frac{1}{1 + j3.8} + \frac{j}{4} \right] \mathbf{V}_1 + \left[ \frac{1}{j4} - \frac{1}{1 + j3.8} \right] \mathbf{V}_2 = -5\angle -18^\circ \quad [1]$$

$$\left[ \frac{1}{j4} - \frac{1}{1 + j3.8} \right] \mathbf{V}_1 + \left[ \frac{1}{2} + \frac{1}{1 + j3.8} + \frac{j}{4} \right] \mathbf{V}_2 = 2\angle 5^\circ \quad [2]$$

Solving,

$$\mathbf{V}_1 = 9.60\angle -115.9^\circ \text{ V}$$

$$\mathbf{V}_2 = 3.13\angle -10.1^\circ \text{ V}$$

And

$$\mathbf{I}_B = \frac{\mathbf{V}_1 - \mathbf{V}_2}{1 + j3.8} = 2.77\angle 153^\circ \text{ A}$$

54. By nodal analysis, we may write

$$-15\angle 0^\circ = \frac{\mathbf{V}_1}{j2} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{1 + j3.8} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{-j4} \quad [1]$$

$$25\angle 131^\circ = \frac{\mathbf{V}_2}{2} + \frac{\mathbf{V}_2 - \mathbf{V}_1}{-j4} + \frac{\mathbf{V}_2 - \mathbf{V}_1}{1 + j3.8} \quad [2]$$

Grouping terms,

$$\left[ \frac{1}{j2} + \frac{1}{1 + j3.8} + \frac{j}{4} \right] \mathbf{V}_1 - \left[ \frac{1}{1 + j3.8} - \frac{1}{j4} \right] \mathbf{V}_2 = -15 \quad [1]$$

$$\left[ \frac{1}{j4} - \frac{1}{1 + j3.8} \right] \mathbf{V}_1 + \left[ \frac{1}{2} + \frac{1}{1 + j3.8} + \frac{j}{4} \right] \mathbf{V}_2 = 25\angle 131^\circ \quad [2]$$

Solving,

$$\mathbf{V}_1 = 34.2\angle -103.5^\circ \text{ V}$$

$$\mathbf{V}_2 = 41.91\angle 134.8^\circ \text{ V}$$

55. Define  $\mathbf{I}_1, \mathbf{I}_2, \mathbf{I}_x$  and apply mesh analysis:

$$-4\angle 0 + (2 + 4.7)\mathbf{I}_1 + j2(\mathbf{I}_1 - \mathbf{I}_2) = 0 \quad [1]$$

$$-(2 + 4.7 - j5)\mathbf{I}_2 - 4.7\mathbf{I}_1 - 2\mathbf{I}_x = 0 \quad [2]$$

$$(1 + 2 + j2)\mathbf{I}_x - j2\mathbf{I}_1 + 2\mathbf{I}_2 = 0 \quad [3]$$

Solving,

$$\mathbf{I}_x = 0.206\angle 81^\circ \text{ A}$$

so

$$\mathbf{V}_x = (1)\mathbf{I}_x = 0.206\angle 81^\circ \text{ V}$$

and

$$v_x(t) = 0.206 \cos(20t + 81^\circ) \text{ V}$$

56. Define  $\mathbf{I}_1, \mathbf{I}_2, \mathbf{I}_x$  and apply mesh analysis:

$$-4\angle 0 + (2 + 4.7)\mathbf{I}_1 + j2(\mathbf{I}_1 - \mathbf{I}_2) = 0 \quad [1]$$

$$-(2 + 4.7 - j5)\mathbf{I}_2 - 4.7\mathbf{I}_1 - 2\mathbf{I}_x = 0 \quad [2]$$

$$(1 + 2 + j2)\mathbf{I}_x - j2\mathbf{I}_1 + 2\mathbf{I}_2 = 0 \quad [3]$$

Solving,

$$\mathbf{I}_x = 0.206\angle 81^\circ \text{ A}$$

so

$$i_x(t) = 0.206 \cos(20t + 81^\circ) \text{ A}$$

57.

$$\mathbf{V}_1 = 133\angle 77^\circ \text{ V}$$

$$\mathbf{V}_2 = 55\angle 22^\circ \text{ V}$$

So

$$-133\angle 77^\circ + 0.8\mathbf{I}_1 + j0.312\mathbf{I}_1 - j0.392\mathbf{I}_2 = 0 \quad [1]$$

$$(j0.392 - j0.714 + j0.448)\mathbf{I}_2 - j0.392\mathbf{I}_1 + j0.714\mathbf{I}_4 - j0.448\mathbf{I}_3 = 0 \quad [2]$$

$$(0.6 + j0.448)\mathbf{I}_3 - j0.448\mathbf{I}_2 + 55\angle 22^\circ = 0 \quad [3]$$

$$(0.4 - j0.714)\mathbf{I}_4 + j0.714\mathbf{I}_2 = 0 \quad [4]$$

Solving,

$$\mathbf{I}_1 = 165\angle 72.6^\circ \text{ A}$$

$$\mathbf{I}_2 = 138\angle 73.5^\circ \text{ A}$$

$$\mathbf{I}_3 = 148\angle 144.8^\circ \text{ A}$$

$$\mathbf{I}_4 = 129\angle 115.6^\circ \text{ A}$$

and

$$i_1(t) = 165 \cos(14t + 72.6^\circ) \text{ A}$$

$$i_2(t) = 138 \cos(14t + 73.5^\circ) \text{ A}$$

$$i_3(t) = 148 \cos(14t + 144.8^\circ) \text{ A}$$

$$i_4(t) = 129 \cos(14t + 115.6^\circ) \text{ A}$$

58

$$\mathbf{V}_1 = 0.009 \angle 0.5^\circ \text{ V}$$

$$\mathbf{V}_2 = 0.004 \angle 1.5^\circ \text{ V}$$

$$\omega = 500 \text{ rad/s}$$

So

$$28 \text{ mH} \rightarrow j14 \ \Omega$$

$$100 \text{ mF} \rightarrow -j0.02 \ \Omega$$

$$32 \text{ mH} \rightarrow j16 \ \Omega$$

Thus, defining  $\mathbf{V}_3$  and  $\mathbf{V}_4$ ,

$$0 = \frac{\mathbf{V}_3 - \mathbf{V}_1}{0.8} + \frac{\mathbf{V}_3}{j14} + \frac{\mathbf{V}_3 - \mathbf{V}_4}{0.4} + \frac{\mathbf{V}_3 - \mathbf{V}_4}{-j0.02} \quad [1]$$

$$0 = \frac{\mathbf{V}_4 - \mathbf{V}_2}{0.6} + \frac{\mathbf{V}_4}{j16} + \frac{\mathbf{V}_4 - \mathbf{V}_3}{-j0.02} + \frac{\mathbf{V}_4 - \mathbf{V}_3}{0.4} \quad [2]$$

Grouping terms,

$$-\frac{1}{0.8} \mathbf{V}_1 + \left( \frac{1}{0.8} + \frac{1}{j14} + \frac{1}{0.4} - \frac{1}{j0.02} \right) \mathbf{V}_3 + \left( \frac{1}{j0.02} - \frac{1}{0.4} \right) \mathbf{V}_4 = 0$$

$$-\frac{1}{0.6} \mathbf{V}_2 + \left( \frac{1}{j0.02} - \frac{1}{0.4} \right) \mathbf{V}_3 + \left( \frac{1}{0.6} + \frac{1}{j16} - \frac{1}{j0.02} + \frac{1}{0.4} \right) \mathbf{V}_4 = 0$$

Solving,

$$\mathbf{V}_3 = 3.55 \times 10^{-4} \angle -84.2^\circ \text{ V}$$

$$\mathbf{V}_4 = 1.30 \times 10^{-4} \angle -83.8^\circ \text{ V}$$

so

$$v_3(t) = 3.55 \times 10^{-4} \cos(500t - 84.2^\circ) \text{ V}$$

$$v_4(t) = 1.30 \times 10^{-4} \cos(500t - 83.8^\circ) \text{ V}$$

59. (a)

$$\mathbf{V}_o = A\mathbf{V}_i \text{ so } \mathbf{V}_i = \frac{\mathbf{V}_o}{A} \quad [1]$$

Then,

$$\frac{\mathbf{V}_o - \mathbf{V}_i}{R_f} \left( \frac{-j}{\omega C_1} \right) = \left[ \frac{\mathbf{V}_i - \mathbf{V}_s}{\frac{-j}{\omega C_1}} \right] \quad [2]$$

Using Eq. [1] to eliminate  $\mathbf{V}_i$  in Eq. [2] yields

$$\mathbf{V}_o \left( \frac{j}{A\omega C_1} - \frac{j}{\omega C_1} - \frac{R_f}{A} \right) = \mathbf{V}_s R_f$$

Thus,

$$\frac{\mathbf{V}_o}{\mathbf{V}_s} = - \frac{R_f}{\left[ -\frac{R_f}{A} + j \left( \frac{1}{A\omega C_1} - \frac{1}{\omega C_1} \right) \right]}; \text{ As } A \rightarrow \infty, \frac{\mathbf{V}_o}{\mathbf{V}_s} \rightarrow \frac{-R_f}{\frac{-j}{\omega C_1}} = -j\omega R_f C_1$$

(b)

 $\mathbf{V}_o = A\mathbf{V}_i$  as before.

$$\mathbf{Z}_f = R_f \parallel \frac{1}{j\omega C_f} = \frac{R_f}{1 + j\omega R_f C_f}$$

Then,

$$(\mathbf{V}_o - \mathbf{V}_i) \left( \frac{-j}{\omega C_1} \right) = (\mathbf{V}_i - \mathbf{V}_s) \mathbf{Z}_f$$

Eliminating  $\mathbf{V}_i$  and collecting terms,

$$\mathbf{V}_o \left[ \left( 1 - \frac{1}{A} \right) \left( \frac{-j}{\omega C_1} \right) - \frac{\mathbf{Z}_f}{A} \right] = -\mathbf{V}_s \frac{\mathbf{Z}_f}{A}$$

Or, substituting in  $\mathbf{Z}_f$ ,

$$\frac{\mathbf{V}_o}{\mathbf{V}_s} = - \frac{\frac{R_f}{1 + j\omega R_f C_f}}{\left( 1 - \frac{1}{A} \right) \left( \frac{-j}{\omega C_1} \right) - \frac{1}{A} \left[ \frac{R_f}{1 + j\omega R_f C_f} \right]}$$

$$\text{As } A \rightarrow \infty, \frac{\mathbf{V}_o}{\mathbf{V}_s} \rightarrow \frac{-\frac{R_f}{1 + j\omega R_f C_f}}{\frac{-j}{\omega C_1}} = -\frac{j\omega R_f C_1}{1 + j\omega R_f C_f}$$

60.  $250 \text{ mF} \rightarrow -j0.2 \Omega$   
 $70 \text{ mH} \rightarrow j1.4 \Omega$   
 $9 \cos 20t \text{ V} \rightarrow 9 \angle 0^\circ \text{ V}$   
 $9 \sin 20t \text{ V} \rightarrow 9 \angle -90^\circ \text{ V}$

Mesh equations:

$$(3 - j0.2)\mathbf{I}_1 + j0.2\mathbf{I}_2 - 3\mathbf{I}_3 = 9 \angle 0^\circ$$

$$0.005\mathbf{I}_1 + j0.2\mathbf{I}_1 + (j1.4 - j0.2)\mathbf{I}_2 - j1.4\mathbf{I}_4 = 0$$

$$-3\mathbf{I}_1 + (3 - j0.2)\mathbf{I}_3 + j0.2\mathbf{I}_4 = -9 \angle -90^\circ$$

$$-j1.4\mathbf{I}_2 + j0.2\mathbf{I}_3 + (5 + j1.4 - j0.2)\mathbf{I}_4 = 9 \angle -90^\circ$$

*Solving,*

$$\mathbf{I}_1 = 27.1 \angle 132.5^\circ \text{ A}$$

$$\mathbf{I}_2 = 6.14 \angle -34^\circ \text{ A}$$

$$\mathbf{I}_3 = 29.2 \angle 132.5^\circ \text{ A}$$

$$\mathbf{I}_4 = 1.82 \angle -0.6^\circ \text{ A}$$

Hence,

$$i_1(t) = 27.1 \cos(20t + 132.5^\circ) \text{ A}$$

$$i_2(t) = 6.14 \cos(20t - 34^\circ) \text{ A}$$

$$i_3(t) = 29.2 \cos(20t + 132.5^\circ) \text{ A}$$

$$i_4(t) = 1.82 \cos(20t - 0.6^\circ) \text{ A}$$

61. Scaling to mA and k $\Omega$ , we can write two nodal equations:

$$3\angle -41^\circ = \frac{V_{1a}}{3} - \frac{V_{1a}}{j3} + \frac{V_{1a} - V_{2a}}{j8} + \frac{V_{1a} - V_{2a}}{3}$$

$$0 = \frac{V_{2a}}{3} - \frac{V_{2a}}{j2} + \frac{V_{2a} - V_{1a}}{-j5} + \frac{V_{2a} - V_{1a}}{j8}$$

Grouping terms and solving,

$$V_{1a} = 4.20\angle -8.4^\circ \text{ V}$$

$$V_{2a} = 0.584\angle 133.5^\circ \text{ V}$$

We now replace the  $3\angle -41^\circ$  source with 0, and set the second equation to  $-5\angle 13^\circ$

Then,

$$V_{1b} = 0.973\angle -74.5^\circ \text{ V}$$

$$V_{2b} = 9.12\angle -115^\circ \text{ V}$$

Note that

$$V_1 = V_{1a} + V_{1b}$$

$$V_2 = V_{2a} + V_{2b}$$

62. We can write two nodal equations:

$$33\angle 3^\circ - 51\angle -91^\circ = \frac{\mathbf{V}_1}{j3} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{-j5}$$

$$51\angle -91^\circ = \frac{\mathbf{V}_2}{2} + \frac{\mathbf{V}_2 - \mathbf{V}_1}{-j5}$$

Which may be solved to yield

$$\mathbf{V}_1 = 391\angle 108.3^\circ \text{ mV}$$

$$\mathbf{V}_1 = 198\angle -156.7^\circ \text{ mV}$$

63. Here, we must employ superposition and recompute impedances each time.

$$\mathbf{I}_1 = 0.004\angle 0 \text{ A at } \omega = 40 \text{ rad/s and } \mathbf{I}_1 = 0.004\angle -90^\circ \text{ A at } \omega = 30 \text{ rad/s}$$

$$j3 = j\omega L = j2.5L \text{ so } L = 3 / 2.5 = 1.2 \text{ H}$$

This represents an impedance of  $j48 \Omega$  at  $\omega = 40 \text{ rad/s}$  and  $j36 \Omega$  at  $\omega = 30 \text{ rad/s}$

Then

$$-j5 = \frac{-j}{\omega C} = \begin{cases} -j0.3125 \Omega, \omega = 40 \text{ rad/s} \\ -j0.417 \Omega, \omega = 30 \text{ rad/s} \end{cases}$$

Then,

$$0.004\angle 0 = \frac{\mathbf{V}_{1a}}{j48} + \frac{\mathbf{V}_{1a} - \mathbf{V}_{2a}}{-j0.3125}$$

$$0 = \frac{\mathbf{V}_{2a}}{2} + \frac{\mathbf{V}_{2a} - \mathbf{V}_{1a}}{-j0.3125}$$

Solving,

$$\mathbf{V}_{1a} = 0.00814\angle -6.5^\circ \text{ V}$$

$$\mathbf{V}_{2a} = 0.00804\angle 2.4^\circ \text{ V}$$

Then, for the other frequency,

$$0 = \frac{\mathbf{V}_{1b}}{j36} + \frac{\mathbf{V}_{1b} - \mathbf{V}_{2b}}{-j0.417}$$

$$0.004\angle -90^\circ = \frac{\mathbf{V}_{2b}}{2} + \frac{\mathbf{V}_{2b} - \mathbf{V}_{1b}}{-j0.417}$$

Solving,

$$\mathbf{V}_{1b} = 0.00808\angle -86.8^\circ \text{ V}$$

$$\mathbf{V}_{2b} = 0.00799\angle -86.8^\circ \text{ V}$$

64. Open circuit both sources, then remove the  $2 - j \Omega$  impedance and look into the open terminals:

$$\mathbf{Z}_{Th} = j2 + 4\angle 10^\circ = 4.77\angle 34.4^\circ \Omega$$

Next, we re-activate the two current sources and compute the voltage across the open terminals:

$$\mathbf{V}_{oc} = (1.5\angle 24^\circ)(j2) - (-2\angle 38^\circ)(4\angle 10^\circ) = 9.62\angle 64.6^\circ \text{ V}$$

$$\text{Then } \mathbf{I}_1 = (\mathbf{V}_{oc})/[\mathbf{Z}_{th} + (2 - j)] = \frac{\mathbf{V}_{oc}}{\mathbf{Z}_{Th} + (2 - j)} = \frac{9.62\angle 64.6^\circ}{4.77\angle 34.4^\circ + 2 - j} = 1.56\angle 48.7^\circ \text{ A}$$

65. Starting with the left-hand source, we obtain a voltage source

$$(1.5\angle 24^\circ)(j2) = 3\angle 114^\circ \text{ V in series with the impedance } j2 \Omega.$$

Moving to the right-hand source, we replace it along with the  $4\angle 10^\circ \Omega$  impedance by a voltage source

$$(-2\angle 38^\circ)(4\angle 10^\circ) = 8\angle -132^\circ \text{ V in series with the impedance } 4\angle 10^\circ \Omega.$$

Both of these combinations appear in series with the  $1 + j \Omega$  impedance, so

$$\mathbf{I} = (3\angle 114^\circ - 8\angle -132^\circ)(j2 + 1 + j + 4\angle 10^\circ) = \boxed{1.56\angle 27.8^\circ \text{ A}}$$

66. (a)

$$\mathbf{Z}_{Th} = (12 - j34) \parallel j10 = \frac{(12 - j34)(j10)}{12 - j24} = 13.4 \angle 82.9^\circ \Omega$$

and

$$\mathbf{V}_{oc} = (22 \angle 30^\circ)(13.4 \angle 82.9^\circ) = 295 \angle 113^\circ \text{ V}$$


(b) Short-circuiting the two open terminals leads to (by inspection):

$$\mathbf{I}_N = 22 \angle 30^\circ \text{ A}; \text{ From above, } \mathbf{Z}_{th} = 13.4 \angle 82.9^\circ \Omega$$

(c) Utilize the Norton equivalent:

$$\mathbf{I} = (22 \angle 30^\circ) \frac{13.4 \angle 82.9^\circ}{13.4 \angle 82.9^\circ + 7 - j2} = 0.942 \angle 30.4^\circ \text{ A}$$

67. (a) Redrawn:

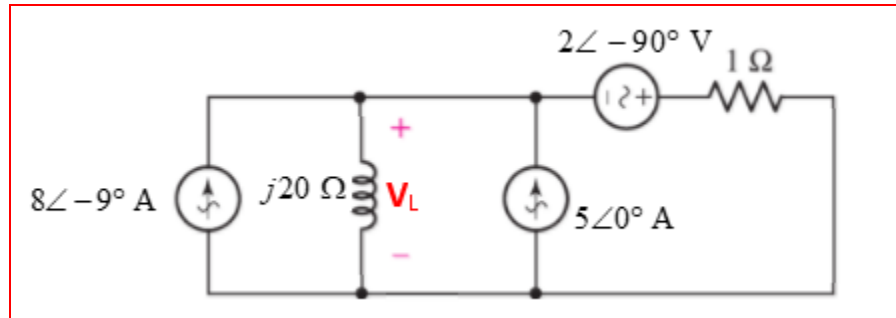

(b) Combining current sources, we may write (with the assistance of a quick source transformation):

$$8\angle -9^\circ + 5\angle 0 = 12.96\angle -5.5^\circ \text{ A}$$

$$12.96\angle -5.5^\circ - \left( \frac{2\angle -90^\circ}{1} \right) = 12.92\angle 3.3^\circ \text{ A}$$

and hence,

by current division,

$$I_L = 12.92\angle 3.3^\circ \left( \frac{1}{1 + j20} \right) = 0.645\angle -83.8^\circ \text{ A}$$

(c)  $V_L = I_L(j20) = 12.9\angle 6.3^\circ \text{ V}$

(d)

```

--- AC Analysis ---
frequency:      0.6366      Hz
V(n001):        mag: 12.9038 phase: 6.16249°      voltage
I(L1):          mag: 0.645212 phase: -83.8346°     device_current
I(I1):          mag: 12.92 phase: 3.3°             device_current
I(R1):          mag: 12.9038 phase: 6.16249°     device_current
    
```

.ac list 0.6366

68. Apply superposition, beginning with the  $3\angle 0$  A source:

Nodal analysis yields

$$0 = \frac{\mathbf{V}_x}{j} + \frac{\mathbf{V}_x - \mathbf{V}_y}{-j} + \frac{\mathbf{V}_x}{1} \quad [1]$$

$$-3\angle 0 = \frac{\mathbf{V}_y - \mathbf{V}_x}{-j} + \frac{\mathbf{V}_y}{2} \quad [2]$$

Grouping terms,

$$\mathbf{V}_x - j\mathbf{V}_y = 0$$

$$-j\mathbf{V}_x + (0.5 + j)\mathbf{V}_y = -3$$

Solving,

$$\mathbf{V}_x = 1.664\angle -124^\circ \text{ V}$$

$$\mathbf{V}_y = 1.664\angle 146^\circ \text{ V}$$

For the  $2.1\angle 0$  V source, we note that  $(1) \parallel (2 - j) = 0.707\angle -8.1^\circ \Omega$ .

$$\text{Then, } \mathbf{V}_A = \frac{(2.1\angle 0)(j)}{j + 0.707\angle -8.1^\circ} = 1.84\angle 37.9^\circ \text{ V}$$

$$\mathbf{V} = \mathbf{V}_A - 2.1\angle 0 = 1.3\angle 120^\circ \text{ V.}$$

Finally,

$$\mathbf{V}_1 = 1.664\angle -124^\circ - 1.3\angle 120^\circ \text{ V} = 2.52\angle -96.3^\circ \text{ V}$$

Returning to the time domain,

$$v_1(t) = 2.52 \cos(20t - 96.3^\circ) \text{ V}$$

69. We write two nodal equations:

$$5\angle 0 = \frac{V_1}{-j3.83} + \frac{V_1 - V_2}{1} \quad [1]$$

$$0 = \frac{V_2 - V_1}{1} + \frac{V_2}{-j2} + \frac{V_2 - 110\angle 0}{5} \quad [2]$$

Grouping terms,

$$(1 + j0.3)V_1 - V_2 = 5$$

$$-V_1 + (1 + j0.5 + 0.2)V_2 = \frac{110}{5}$$

Solving,

$$V_1 = 32.63\angle -81.6^\circ \text{ V, or in the time domain, } v_1(t) = 32.63 \cos(20t - 81.6^\circ) \text{ V}$$


$$V_2 = 32.27\angle -72.9^\circ \text{ V, or in the time domain, } v_2(t) = 32.27 \cos(20t - 72.9^\circ) \text{ V}$$

Therefore,

$$V_{1\Omega} = V_1 - V_2 = 4.90\angle -163^\circ \text{ V}$$

We proceed:
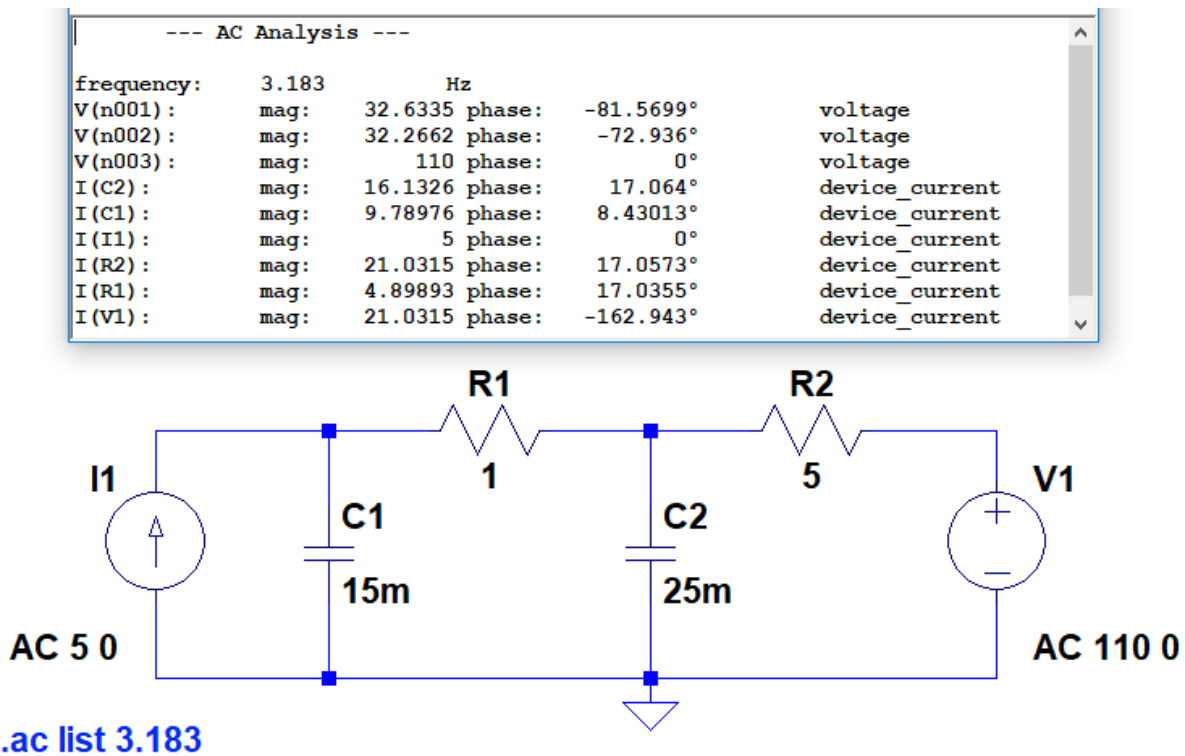
$$P_{1\Omega} = \frac{(v_{1\Omega}(t))^2}{1} = 24.01 \cos^2(20t - 163^\circ) \text{ W}$$



70. We create the following impedances: 2 H becomes  $j2 \Omega$ , and 1 F becomes  $-j \Omega$ . Apply a 1 A test source to the output terminals.

Then,

$$-0.25\mathbf{V}_L = \frac{\mathbf{V}_D}{-j} + \frac{(\mathbf{V}_D - \mathbf{V}_{test})}{j2} \quad [1]$$

$$1 = \frac{(\mathbf{V}_{test} - \mathbf{V}_D)}{j2} \quad [2]$$

$$\mathbf{V}_D - \mathbf{V}_{test} = \mathbf{V}_L \quad [3]$$

So

$$\left(-0.25 - j - \frac{1}{j2}\right)\mathbf{V}_D + \left(0.25 + \frac{1}{j2}\right)\mathbf{V}_{test} = 0$$

$$-\mathbf{V}_D + \mathbf{V}_{test} = j2$$

Solving,

$$\mathbf{V}_{test} = 1.12 \angle 63.4^\circ \text{ V and } \mathbf{Z}_{Th} = 1.12 \angle 63.4^\circ \Omega = 0.50 + j \Omega$$

We may create such an impedance at 1 rad/s by inverting:

$$\frac{1}{\mathbf{Z}_{Th}} = 0.40 - j0.798$$

which can be constructed with  $R = \frac{1}{0.4} = 2.5 \Omega$  in parallel with  $\frac{1}{-j0.798} = j1.25 \Omega$ .

At 1 rad/s, that is a 1.25 H inductor.

Shorting the output terminals,

$$-0.25\mathbf{V}_L + (\mathbf{V}_L - 1)(j) + \frac{\mathbf{V}_L}{j2} = 0$$


Solving,

$$\mathbf{V}_L = 36.7 \angle -172.5^\circ \text{ V}$$


Thus,

$$\mathbf{I}_N = \mathbf{I}_{SC} = \frac{\mathbf{V}_L}{j2} = 18.4 \angle 97.5^\circ \text{ A}$$



71.

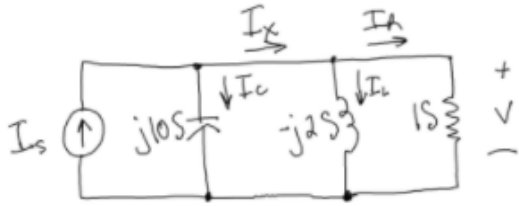

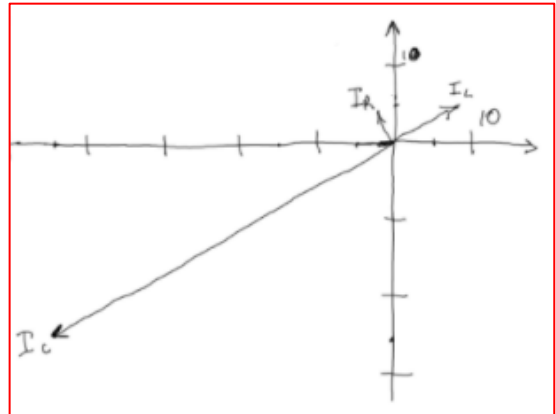a)  $I_R = V(1) = (5 \angle 120^\circ)(1)$   
 $= (-2.5 + j4.33)(1)$   
 $= -2.5 + j4.33 \text{ A} = (5 \angle 120^\circ) \text{ A}$   
 $I_L = (5 \angle 120^\circ)(-j2)$   
 $= 8.66 + j5 \text{ A} = (10 \angle 30^\circ) \text{ A}$   
 $I_C = (5 \angle 120^\circ)(j10)$   
 $= -43.3 - j25 \text{ A} = (50 \angle -150^\circ) \text{ A}$



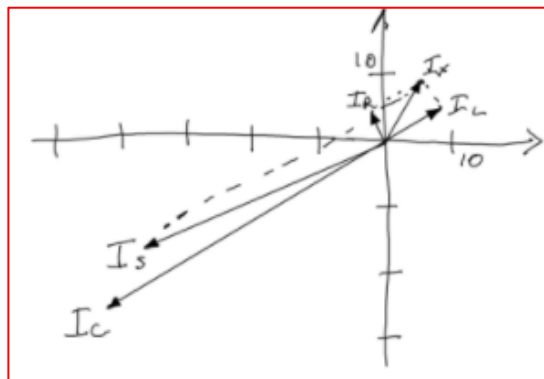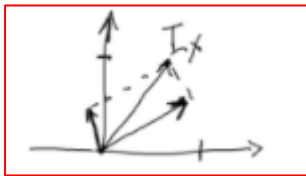b)  $I_x = I_R + I_L = -2.5 + j4.33 + 8.66 + j5$   
 $= 6.16 + j9.33 \text{ A} = (11.18 \angle 56.57^\circ) \text{ A}$   
 $I_s = I_x + I_C$   
 $= -37.14 - j15.67 \text{ A} = (40.31 \angle -157.13^\circ) \text{ A}$



72.  $\mathbf{V}_1 = 100\angle 0^\circ \text{ V}$ ,  $|\mathbf{V}_2| = 140 \text{ V}$ ,  $|\mathbf{V}_1 + \mathbf{V}_2| = 120 \text{ V}$ .  
Let  $50 \text{ V} = 1 \text{ inch}$ . From the sketch, for  $\angle \mathbf{V}_2$  positive,  
 $\mathbf{V}_2 = 140\angle 122.5^\circ$ . We may also have  $\mathbf{V}_2 = 140\angle -122.5^\circ \text{ V}$

[Analytically:  $|100 + 140\angle a| = 120$   
so  $|100 + 140 \cos a + j140 \sin a| = 120$   
Using the “Solve” routine of a scientific calculator,  
 $a = \pm 122.88^\circ$ .]

73. (a) 
$$\mathbf{I}_L = \frac{100}{j2.5 + \frac{-2}{2-j1}} = \frac{100(2-j1)}{2.5+j3} = 57.26\angle -76.76^\circ (2.29in)$$

$$\mathbf{I}_R = (57.26\angle -76.76^\circ) \frac{-j1}{2-j1} = 25.61\angle -140.19^\circ (1.02in)$$


$$\mathbf{I}_C = (57.26\angle -76.76^\circ) \frac{2}{2-j1} = 51.21\angle -50.19^\circ (2.05in)$$

$$\mathbf{V}_L = 2.5 \times 57.26\angle 90^\circ - 76.76^\circ = 143.15\angle 13.24^\circ (2.86in)$$

$$\mathbf{V}_R = 2 \times 25.61\angle -140.19^\circ = 51.22\angle -140.19^\circ (1.02in)$$

$$\mathbf{V}_C = 51.21\angle -140.19^\circ (1.02in)$$

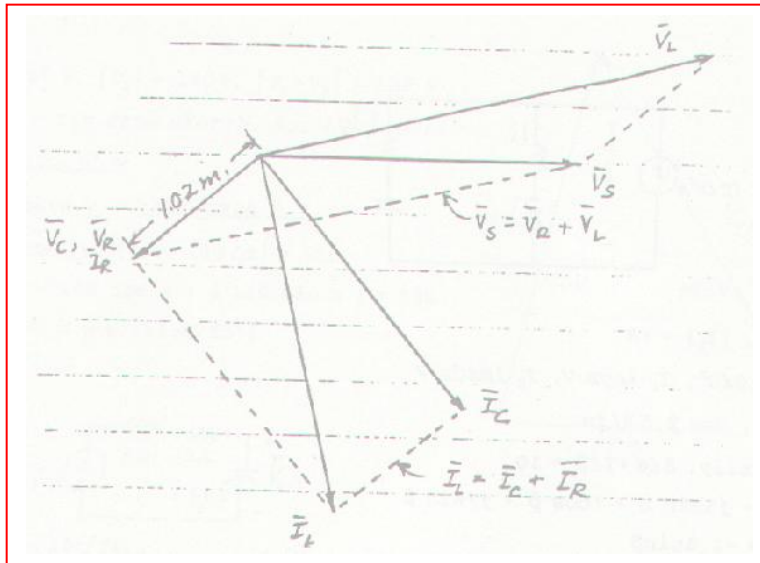(b) Scales (inches) are noted above next to each answer.




74. (a)

$$\mathbf{I}_1 = \frac{120}{40 \angle 30^\circ} = 3 \angle -30^\circ \text{ A}$$

$$\mathbf{I}_2 = \frac{120}{50 - j30} = 2.058 \angle 30.96^\circ \text{ A}$$
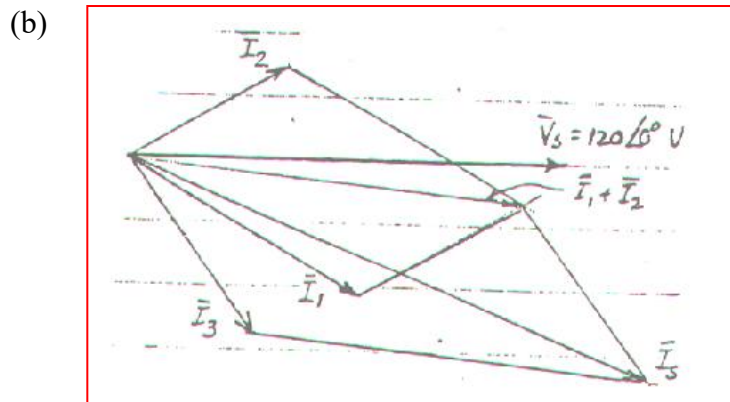
$$\mathbf{I}_3 = \frac{120}{30 + j40} = 2.4 \angle -53.13^\circ \text{ A}$$



(c)

$$\mathbf{I}_s = \mathbf{I}_1 + \mathbf{I}_2 + \mathbf{I}_3$$

$$= 6.265 \angle -22.14^\circ \text{ A}$$

$$75. \quad V_2 = I_c(j2) = (1 \angle 0^\circ)(j2)$$

$$= j2 \text{ V} = (2 \angle 90^\circ) \text{ V}$$

$$I_c = \frac{V_R - V_2}{-j4}$$

$$(1 \angle 0^\circ) = \frac{V_R - (2 \angle 90^\circ)}{-j4}$$

$$V_R = (2 \angle -90^\circ) \text{ V} = -j2 \text{ V}$$

$$I_s = I_R + I_c$$


$$I_s = \frac{V_R}{3} + I_c = (0.67 \angle -90^\circ) + (1 \angle 0^\circ) = 1 + j0.67 \text{ A}$$

$$= (1.2 \angle -33.7^\circ) \text{ A}$$

$$V_1 = 5I_s = 5(1.2 \angle -33.7^\circ)$$

$$= (6.01 \angle -33.7^\circ) \text{ V} = 5 - j3.33 \text{ V}$$

a)

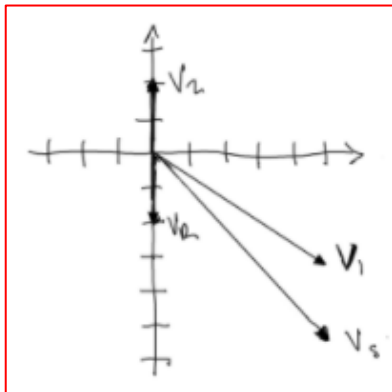b)  $V_2$  to  $V_1$ :

$$\frac{V_2}{V_1} = -0.18 + j0.28$$


76. a)  $X_{L1} = j\omega L = j(20)(100 \cdot 10^{-3}) = j2 \Omega$

$X_{L2} = j(20)(150 \cdot 10^{-3}) = j3 \Omega$

$X_C = \frac{-j}{\omega C} = \frac{-j}{(20)(15 \cdot 10^{-3})} = -j3.33 \Omega$


$V = (5 \angle -78^\circ) \text{ V}$

$I = (2 \angle -45^\circ) \text{ A}$

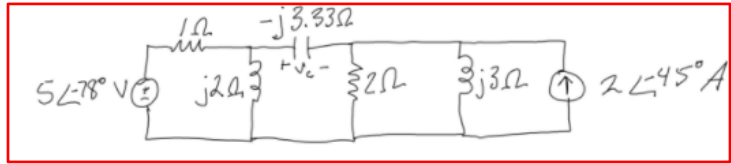

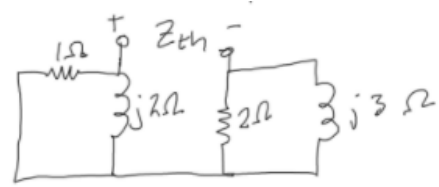b) Short the voltage source and open the current source and make  $Z_{th}$  the impedance across the capacitor.

$Z_{th} = \frac{(1)(j2)}{1+j2} + \frac{(2)(j3)}{2+j3}$   
 $= 0.8 + j0.4 + 1.38 + j0.92$   
 $= 2.18 + j1.32 \Omega = (2.55 \angle 31.2^\circ) \Omega$



Calculate the Thevenin equivalent voltage across the capacitor by open-circuiting the capacitor.

$V_1 = \frac{(1)(j2)}{1+j2} * (5 \angle -78^\circ) =$   
 $= (4.47 \angle -51.43^\circ) \text{ V} = 2.79 - j3.49 \text{ V}$



At node  $V_2$ :

$\frac{V_2}{2} + \frac{V_2}{j3} - (2 \angle -45^\circ) = 0$

$V_2 * (\frac{1}{2} + \frac{1}{j3}) = (2 \angle -45^\circ)$


$V_2 = (3.33 \angle -11.34^\circ) = 3.20 - j0.64 \text{ V}$

$V_{oc} = V_1 - V_2 = 2.79 - j3.49 - (3.20 - j0.64)$

$= (-0.47 - j2.84) \text{ V} = (2.88 \angle -99.46^\circ) \text{ V}$


Thevenin equivalent circuit:

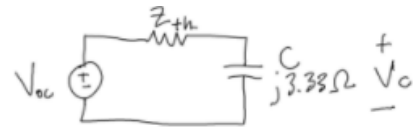$V_c = \frac{-j3.33}{Z_{th} - j3.33} * V_{oc} = (3.23 \angle -146.74^\circ)$



$V_c(t) = 3.23 * \sin(20t - 146.74^\circ) \text{ V}$

c)

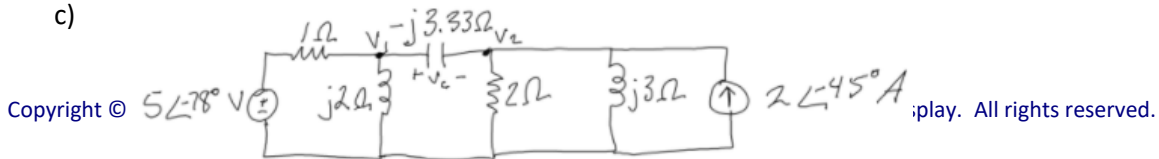

$$\text{Node } V_1: \frac{V_1 - (5 \angle -78^\circ)}{1} + \frac{V_1}{j2} + \frac{V_1 - V_2}{-j3.33} = 0$$

$$V_c = V_1 - V_2$$

$$\frac{V_1 - (5 \angle -78^\circ)}{1} + \frac{V_1}{j2} + \frac{V_c}{-j3.33} = 0$$

$$V_1 * (1 - j0.5) = (5 \angle -78^\circ) + (0.97 \angle 123.46^\circ)$$


$$V_1 = \frac{0.51 + j4.08}{1 - j0.5} = (2.04 - j3.06) \text{ V}$$

$$V_1 = (3.68 \angle -56.34^\circ) \text{ V}$$


$$I_c = \frac{(5 \angle -78^\circ) - V_1}{1} = (5 \angle -78^\circ) - (3.68 \angle -56.34^\circ)$$

$$= (-1.0 - j1.83) \text{ A} = (2.08 \angle -118.69^\circ) \text{ A}$$


d)

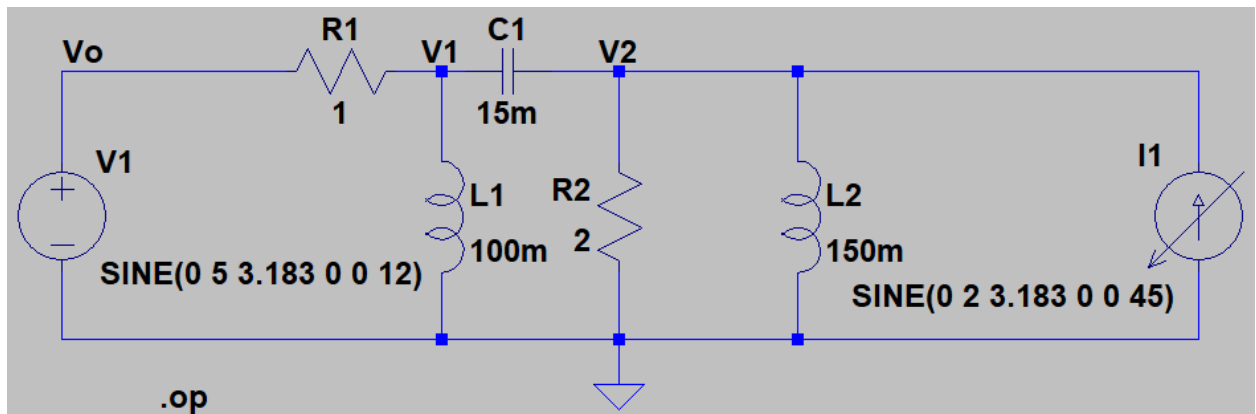

77.

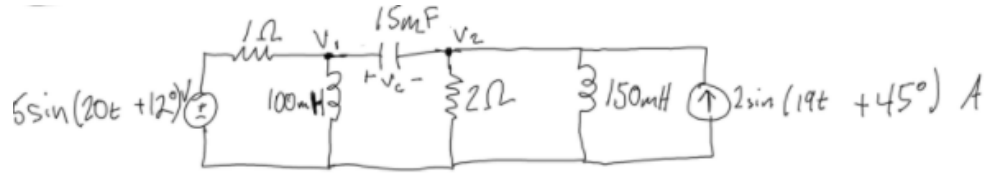

Superposition theorem:

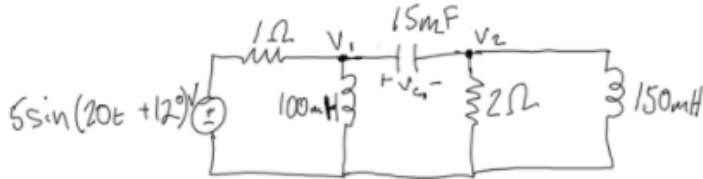


$$X_{L1} = j\omega L = j(20)(100 \cdot 10^{-3}) = j2 \Omega$$

$$X_{L2} = j(20)(150 \cdot 10^{-3}) = j3 \Omega$$

$$X_C = \frac{-j}{\omega C} = \frac{-j}{(20)(15 \cdot 10^{-3})} = -j3.33 \Omega$$
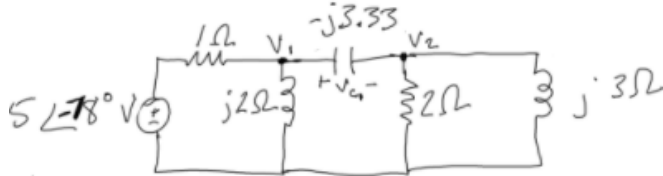
$$5\sin(20t + 12) \rightarrow (5 \angle -78^\circ)$$



Node  $V_1$ :

$$\frac{V_1 - (5 \angle -78^\circ)}{1} + \frac{V_1}{j2} + \frac{V_1 - V_2}{-j3.33} = 0$$

$$V_1 \left( 1 + \frac{1}{j2} - \frac{1}{j3.33} \right) + V_2 \frac{1}{-j3.33} = (5 \angle -78^\circ)$$

$$V_1 (1 - j0.2) + V_2 (-j0.3) = 1.04 - j4.89$$

Node 2:

$$\frac{V_2 - V_1}{-j3.33} + \frac{V_2}{2} + \frac{V_2}{j3} = 0$$

$$V_1 \frac{1}{j3.33} + V_2 \left( \frac{1}{j3} + \frac{1}{2} - \frac{1}{j3.33} \right) = 0$$

$$V_1 (-j0.3) = -V_2 (0.5 - j0.03)$$

$$V_1 = -V_2 \left( \frac{0.5 - j0.03}{-j0.3} \right)$$

$$V_1 = (-0.1 - j1.67) V_2$$

$$(-0.1 - j1.67) V_2 (1 - j0.2) + V_2 (-j0.3) = 1.04 - j4.89$$

$$(-0.43 - j1.95) V_2 = 1.04 - j4.89$$


$$V_2 = 2.28 + j1.04 \text{ V}$$

$$V_1 = (4.19 \angle -68.91^\circ) \text{ V} = (1.51 - j3.91) \text{ V}$$

$$V_{C1} = V_1 - V_2$$

$$= (-0.77 - j4.96) \text{ V} = (5.02 \angle -98.82^\circ) \text{ V}$$

Other side of circuit:

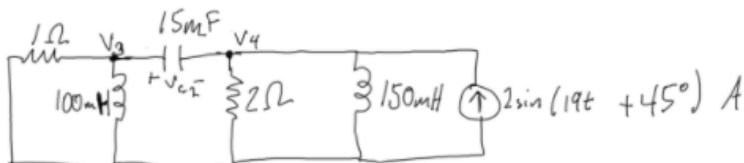


$$X_{L1} = j\omega L = j(19)(100 \cdot 10^{-3}) = j1.9 \Omega$$

$$X_{L2} = j(19)(150 \cdot 10^{-3}) = j2.85 \Omega$$

$$X_c = \frac{-j}{\omega C} = \frac{-j}{(19)(15 \times 10^{-3})} = -j3.51 \Omega$$
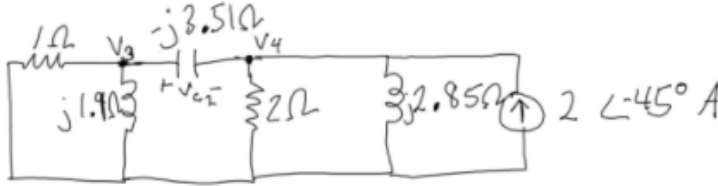
$$2\sin(19t + 45^\circ) \rightarrow (2 \angle -45^\circ) \text{ A}$$



Node  $V_3$ :

$$\frac{V_3}{1} + \frac{V_3}{j1.9} + \frac{V_3 - V_4}{-j3.51} = 0$$

$$V_3(1 - j0.24) + V_4(-j0.29) = 0$$

$$V_4 = V_3 \left( \frac{1 - j0.24}{j0.29} \right) = V_3(-0.85 - j3.51)$$

Node  $V_4$ :

$$\frac{V_4 - V_3}{-j3.51} + \frac{V_4}{2} + \frac{V_4}{j2.85} = (2 \angle -45^\circ)$$

$$V_1(-j0.29) + V_4(0.5 - j0.065) = (1.41 - j1.41)$$

$$V_1(-j0.29) + V_3(-0.85 - j3.51)(0.5 - j0.065) = (1.41 - j1.41)$$

$$V_3 = (0.43 + j0.85) \text{ V}$$

$$V_4 = (2.62 - j2.23) \text{ V}$$

$$V_{c2} = V_3 - V_4$$


$$= (-2.20 - j3.09) \text{ V} = (3.80 \angle 125.42^\circ) \text{ V}$$

$$V_c = V_{c1} + V_{c2}$$

$$= (-2.97 - j1.87) \text{ V} = (3.51 \angle -147.85^\circ) \text{ V}$$

$$\text{Actual: } v_c(t) = 3.51 \cos(\omega t - 147.85^\circ) \text{ V}$$

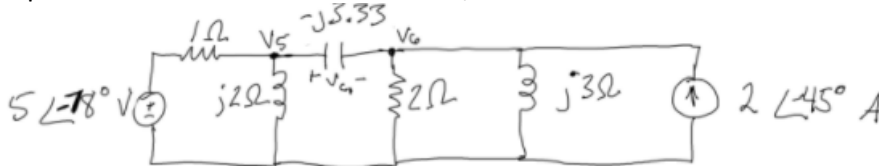Expected will have both sides at 20 rad/s:



Node  $V_5$ :

$$\frac{V_5 - (5 \angle -78^\circ)}{1} + \frac{V_5}{j2} + \frac{V_5 - V_6}{-j3.33} = 0$$

$$V_5(1 - j0.2) + V_6(-j0.3) = 1.04 - j4.89$$

$$V_5 = \frac{(1.04 - j4.89) - V_6(-j0.3)}{1 - j0.2} = (1.94 - j4.50) - (0.058 - j0.29)V_6$$

Node 6:

$$\frac{V_6 - V_5}{-j3.33} + \frac{V_6}{2} + \frac{V_6}{j3} = (2 \angle -45^\circ)$$

$$V_5(-j0.3) + V_6(0.5 - j0.03) = 1.41 - j1.41$$

$$(1.94 - j4.50) - (0.058 - j0.29)V_6(-j0.3) + V_6(0.5 - j0.03) = 1.41 - j1.41$$

$$V_6 = (4.74 - j1.32) \text{ V}$$


$$V_5 = (2.05 - j3.05) \text{ V}$$

$$V_c = V_5 - V_6 =$$

$$= (-2.70 - j1.74) \text{ V} = (3.23 \angle -147.14^\circ)$$

$$\text{Expected: } v_c(t) = 3.23 \cos(20t - 147.14^\circ) \text{ V}$$

78. a)

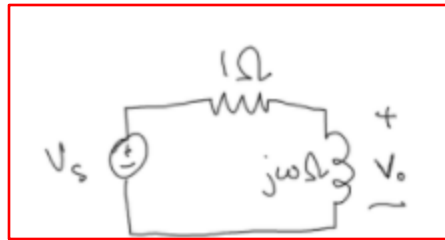

$$b) V_o = \left(\frac{j\omega}{1+j\omega}\right)V_s$$


$$\frac{V_o}{V_s} = \frac{j\omega}{1+j\omega}$$

c) Using MATLAB:

```

Vo = [1 0];
Vs = [1 1];
w=0.01:0.01:100;
y=tf(Vo,Vs);
bode(y,{w})
grid on

```

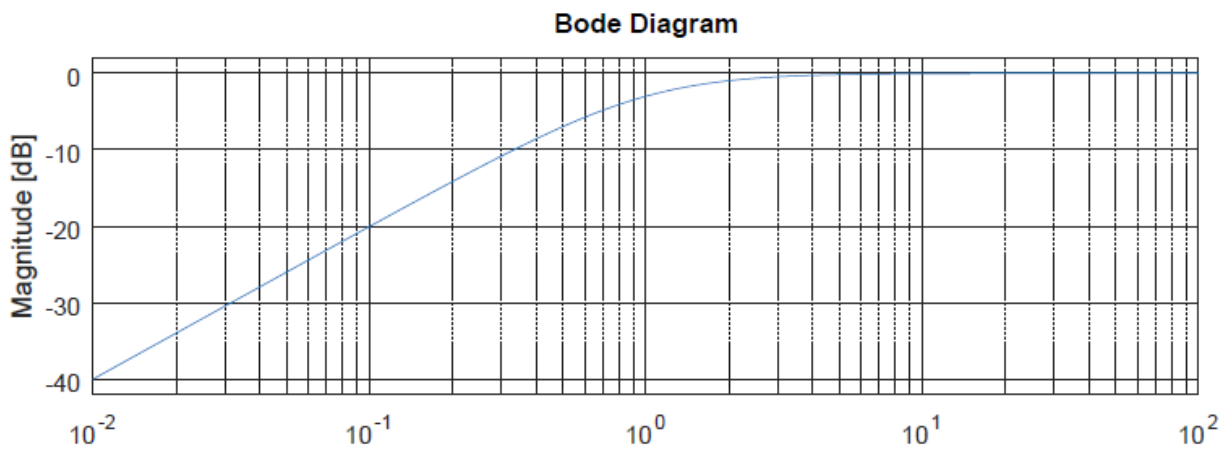


d) Low frequencies are more effectively transferred to the output.

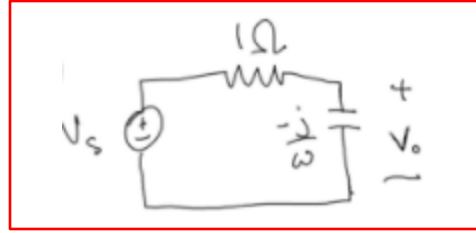79. a)


$$V_o = \left( \frac{-j/\omega}{1-j/\omega} \right) V_s$$

$$\frac{V_o}{V_s} = \frac{-j}{\omega-j} = \frac{1}{1+j\omega}$$



Using MATLAB:
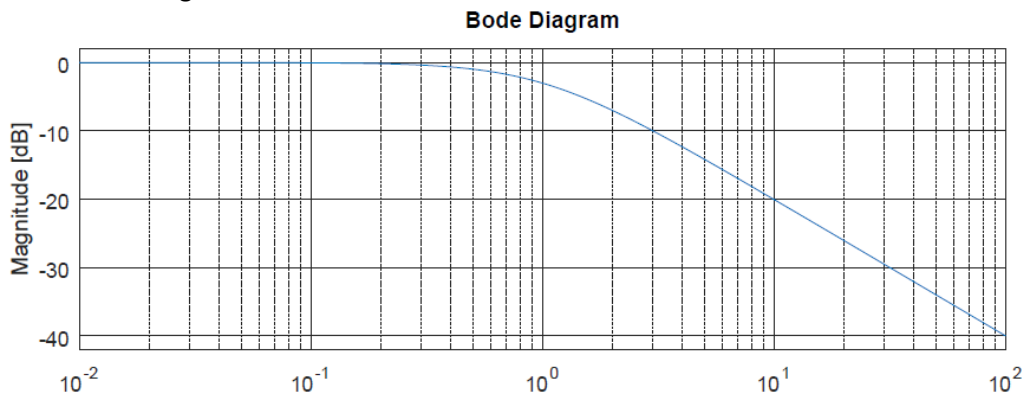
```
Vo = [1];
Vs = [1 1];
w=0.01:0.01:100;
y=tf(Vo,Vs);
bode(y,{w})
grid on
```



Low frequencies are more effectively transferred to the output.

b) One possible solution (DESIGN PROBLEM):

$$\text{Corner frequency: } f_c = \frac{1}{2\pi RC}$$

$$2 \cdot 10^3 = \frac{1}{2\pi RC}$$

$$12.57 \cdot 10^3 = \frac{1}{RC}$$

Choose:  $R = 5 \Omega$ . Then,

$$C = \frac{1}{5(12.57 \cdot 10^3)} = 15.91 \mu\text{F}$$

80. One possible solution (DESIGN PROBLEM):

$$\mathbf{Z} = (0.5 \angle 5.7^\circ) \Omega = 0.498 + j0.0497 \Omega$$

$$F = 628 \text{ Hz}$$

$$\mathbf{Z} = R - jX_c = R - \frac{j}{\omega C}$$

$$= R - \frac{j}{2\pi f C}$$

$$R = 0.50 \Omega$$

$$j0.0497 = \frac{j}{2\pi(628)C}$$

$$C = 5.10 \text{ mF}$$