

Problem Solutions

Chapter Eight: NMOS Logic

P8.1. Consider the NMOS gate depicted in Figure 8.30.

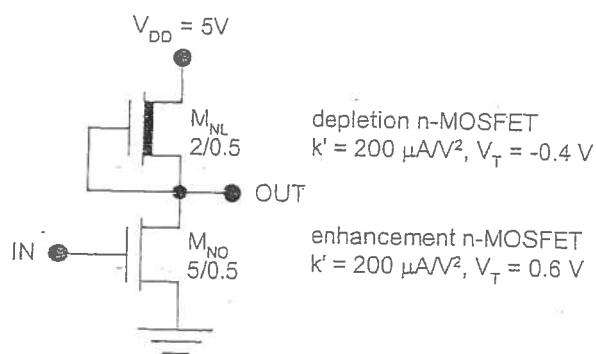


Figure 8.30.

- Determine V_{IL} , V_{IH} , V_{OL} , and V_{OH} .
- Determine the noise margins V_{NML} and V_{NMH} .
- Estimate the average DC dissipation.

Solution.

a. The device transconductance parameters are

$$K_L = \left(\frac{2 \mu m}{0.5 \mu m} \right) 200 \mu A/V^2 = 0.8 mA/V^2 \text{ and}$$

$$K_O = \left(\frac{5 \mu m}{0.5 \mu m} \right) 200 \mu A/V^2 = 2.0 mA/V^2.$$

The four critical voltages are

$$V_{IL} = V_{TO} + \frac{K_L}{\sqrt{K_O K_L + K_O^2}} |V_{TL}|$$

$$= 0.6V + \frac{2.0mA/V^2}{\sqrt{(2.0mA/V^2)(0.8mA/V^2) + (2.0mA/V^2)^2}} |-0.4V| = 0.73V$$

$$V_{IH} = V_{TO} + 2|V_{TL}| \sqrt{\frac{K_L}{3K_O}} = 0.6V + 2|-0.4V| \sqrt{\frac{0.8mA/V^2}{3(2.0mA/V^2)}} = 0.89V,$$

$$V_{OL} = V_{DD} - V_{TO} \pm \sqrt{(V_{DD} - V_{TO})^2 - \left(\frac{K_L}{K_O}\right) V_{TL}^2}$$

, and

$$= 5V - 0.6V \pm \sqrt{(5V - 0.6V)^2 - \left(\frac{0.8mA/V^2}{2.0mA/V^2}\right) (-0.4V)^2} = 0.0073V$$

$$V_{OH} = V_{DD} = 5V.$$

b. The noise margins are

$$V_{NML} = 0.73V - 0.0073V = 0.72V$$

and

$$V_{NMH} = 5V - 0.89V = 4.1V.$$

c. The average dissipation is

$$P_{DC} \approx \frac{P_H + P_L}{2} = \frac{K_L V_{DD} V_{TL}^2}{4} = \frac{(0.8mA/V^2)(5V)(-0.4V)^2}{4} = 0.160mW.$$

P8.2. Consider the NMOS gate of Figure 8.31.

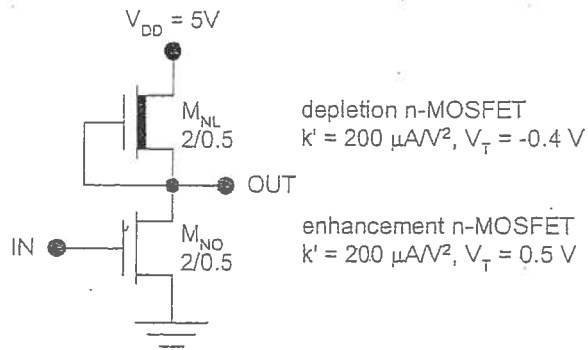


Figure 8.31.

Determine the values of V_{IN} and V_{OUT} for which M_{NO} is at the boundary between saturation and ohmic operation.

Solution. M_{NL} will be saturated so that

$$I_{DD} = \frac{K_L (-V_{TL})^2}{2}$$

For M_{NO} ,

$$I_{DD} = \frac{K_O (V_{IN} - V_{TO})^2}{2}$$

But if M_{NO} is at the boundary between saturated and linear operation, then

$$V_{IN} - V_{TO} = V_{OUT}$$

Hence

$$\frac{K_L (-V_{TL})^2}{2} = \frac{K_O (V_{OUT})^2}{2} \text{ so that}$$

$$V_{OUT} = 0.4V$$

P8.3. Consider the NMOS gate illustrated in Figure 8.32.

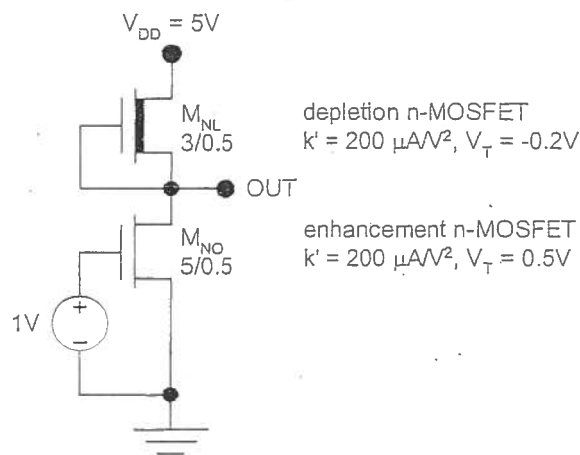


Figure 8.32.

- Determine the mode of operation for each of the transistors.
- Determine the supply current I_{DD} .
- Determine the value of V_{OUT} .

Solution.

- Assume that M_{NO} is linear and M_{NL} is saturated. Then

$$I_{DD} = \frac{1.2mA/V^2}{2} (0.2V)^2 = 0.024mA$$

and

$$V_{OUT} = (1V - 0.5V) - \sqrt{(1V - 0.5V)^2 - \frac{2(0.024mA)}{2mA/V^2}} = 0.025V$$

This is consistent with the starting assumptions.

- The supply current is

$$I_{DD} = 0.024mA$$

c. The output voltage is

$$V_{OUT} = 0.025V.$$

P8.4. Consider the NMOS gate of Figure 8.33.

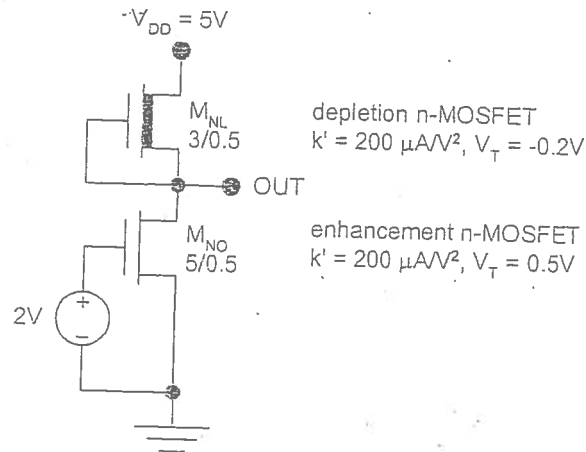


Figure 8.33.

- Determine the mode of operation for each of the transistors.
- Determine the supply current I_{DD} .
- Determine the value of V_{OUT} .

Solution. The device transconductance parameters are given by

$$K_L = \left(\frac{3 \mu m}{0.5 \mu m} \right) 200 \mu A / V^2 = 1.2 mA / V^2 \text{ and}$$

$$K_O = \left(\frac{5 \mu m}{0.5 \mu m} \right) 200 \mu A / V^2 = 2.0 mA / V^2.$$

a. Suppose M_{NL} is saturated but M_{NO} is linear. Then

$$I_{DD} = \frac{(1.2 mA / V^2)(0.2V)^2}{2} = 0.024 mA$$

and

$$V_{OUT} = (2V - 0.5V) - \sqrt{(2V - 0.5V)^2 - \frac{2(0.024mA)}{2.0mA/V^2}} = 0.0080V.$$

Therefore $V_{D50} < V_{G50} - V_{T0}$ but $V_{D5L} > V_{G5L} - V_{TL}$, consistent with the starting assumptions.

b. The supply current is

$$I_{DD} = 0.024mA.$$

c. The output voltage is

$$V_{OUT} = 0.0080V.$$

P8.5. Consider the NMOS gate illustrated in Figure 8.34.

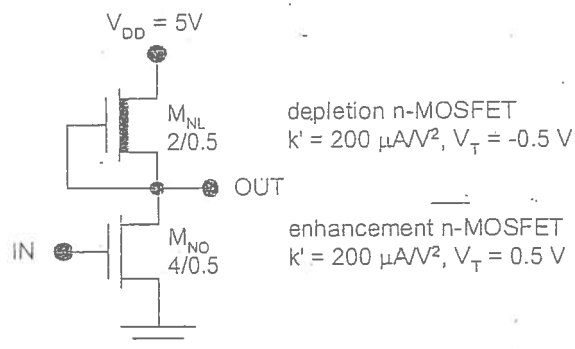


Figure 8.34.

- Using hand calculations, determine and plot the voltage transfer characteristic for the inverter.
- Determine the range of V_{IN} for each mode of operation (cutoff, saturation, and linear) of M_{NO} .

Solution. The device transconductance parameters are given by

$$K_L = \left(\frac{2\mu m}{0.5\mu m} \right) 200 \mu A/V^2 = 0.8mA/V^2 \text{ and}$$

$$K_O = \left(\frac{4 \mu\text{m}}{0.5 \mu\text{m}} \right) 200 \mu\text{A}/V^2 = 1.6 \text{mA}/V^2.$$

For $V_{IN} \leq 0.5V$, M_{NO} is cut off and M_{NL} is linear, so that

$$V_{OUT} = 5V \quad (V_{IN} \leq 0.5V).$$

If $(V_{OUT} + 0.5V) \leq V_{IN} \leq 0.5V$ and $V_{OUT} \geq 4.5V$, M_{NO} is saturated and M_{NL} is linear so that

$$I_{DD} = \frac{K_O}{2} (V_{IN} - V_{TO})^2, \text{ and}$$

$$\begin{aligned} V_{OUT} = V_{DD} - V_{DSL} = V_{DD} - \left[-V_{TL} - \sqrt{(-V_{TL})^2 - \frac{K_O (V_{IN} - V_{TO})^2}{K_L}} \right] \\ = 4.5V + \sqrt{(0.5V)^2 - (2)(V_{IN} - 0.5V)^2}; \\ [(V_{OUT} + 0.5V) \leq V_{IN} \leq 0.5V] \text{ and } [V_{OUT} \geq 4.5V] \end{aligned}$$

Finally, if M_{NO} is linear and M_{NL} is saturated then

$$I_{DD} = \frac{K_L}{2} (-V_{TL})^2, \text{ and}$$

$$\begin{aligned} V_{OUT} = V_{DSO} = (V_{IN} - V_{TO}) - \sqrt{(V_{IN} - V_{TO})^2 - \frac{K_L (-V_{TL})^2}{K_O}} \\ = V_{IN} - 0.5V - \sqrt{(V_{IN} - 0.5V)^2 - (-0.5)^2 / 2}; \\ [(V_{OUT} + 0.5V) \geq V_{IN}] \text{ and } [V_{OUT} \leq 4.5V] \end{aligned}$$

The voltage transfer characteristic appears in Figure 8.40.

 


Figure 8.40.

b. The ranges of V_{IN} for each mode of operation (cutoff, saturation, and linear) of M_{NO} are as follows:

M_{NO} is cutoff for $V_{IN} \leq 0.5V$.

M_{NO} is saturated for $0.5 \leq V_{IN} \leq 0.853V$.

M_{NO} is linear for $0.853 \leq V_{IN}$.

P8.6. Consider the NMOS gate shown in Figure 8.35.

 


Figure 8.35.

- a. Determine the value of V_{OUT} if $V_A = 5V$ and $V_B = V_C = 0V$. (This is the worst case of V_{OL} .)
- b. Determine the value of V_{OUT} if $V_A = V_B = V_C = 5V$.

Solution.

- a. With $V_{INA} = 5V$ and $V_{INB} = V_{INC} = 0V$,

$$\begin{aligned} V_{OL}(\text{one transistor on}) &= V_{DD} - V_{TO} - \sqrt{(V_{DD} - V_{TO})^2 - \left(\frac{K_L}{K_O}\right) V_{TL}^2} \\ &= 5V - 0.6V - \sqrt{(5V - 0.6V)^2 - \left(\frac{1.5/0.5}{2/0.5}\right) (-0.3V)^2} = 0.0075V \end{aligned}$$

- b. With $V_{INA} = V_{INB} = V_{INC} = 5V$,

$$\begin{aligned} V_{OL}(\text{3 transistors on}) &= V_{DD} - V_{TO} - \sqrt{(V_{DD} - V_{TO})^2 - \left(\frac{K_L}{3K_O}\right) V_{TL}^2} \\ &= 5V - 0.6V - \sqrt{(5V - 0.6V)^2 - \left(\frac{1.5/0.5}{(3)2/0.5}\right) (-0.3V)^2} = 0.0025V \end{aligned}$$

P8.7. Consider the NMOS NAND3 gate illustrated in Figure 8.36.

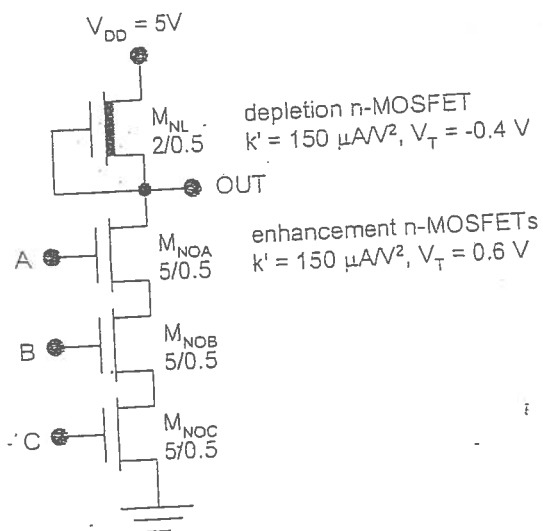


Figure 8.36.

Determine the value of V_{OL} .

Solution. For the NAND3 gate,

$$\begin{aligned}
 V_{OL} &= V_{DD} - V_{TO} - \sqrt{(V_{DD} - V_{TO})^2 - 3 \left(\frac{K_L}{K_O} \right) V_{TL}^2} \\
 &= 5V - 0.6V - \sqrt{(5V - 0.6V)^2 - 3 \left(\frac{5}{2} \right) (-0.4V)^2} = 0.138V
 \end{aligned}$$

P8.8. Consider the NMOS gate depicted in Figure 8.37.

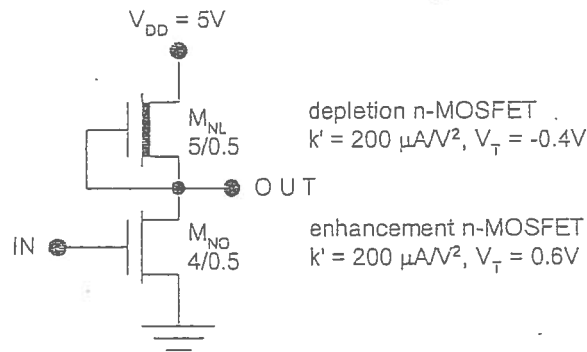


Figure 8.37.

- Using hand calculations, determine V_{IL} , V_{IH} , V_{OL} , and V_{OH} .
- Using SPICE, determine and plot the voltage transfer characteristic for the gate.
- From the tabulated SPICE results, determine the critical voltages and compare these to the values found in (a).

Solution.

- The device transconductance parameters are given by

$$K_L = \left(\frac{5 \mu\text{m}}{0.5 \mu\text{m}} \right) 200 \mu\text{A}/\text{V}^2 = 2.0 \text{mA}/\text{V}^2 \text{ and}$$

$$K_O = \left(\frac{4 \mu\text{m}}{0.5 \mu\text{m}} \right) 200 \mu\text{A}/\text{V}^2 = 1.6 \text{mA}/\text{V}^2.$$

The four critical voltages are

$$\begin{aligned} V_{IL} &= V_{TO} + \frac{K_L}{\sqrt{K_O K_L + K_O^2}} |V_{TL}| \\ &= 0.6\text{V} + \frac{2.0 \text{mA}/\text{V}^2}{\sqrt{(1.6 \text{mA}/\text{V}^2)(2.0 \text{mA}/\text{V}^2) + (1.6 \text{mA}/\text{V}^2)^2}} |-0.4\text{V}| = 0.93\text{V} \end{aligned}$$

$$V_{IH} = V_{TO} + 2|V_{TL}| \sqrt{\frac{K_L}{3K_O}} = 0.6V + 2|-0.4V| \sqrt{\frac{2.0mA/V^2}{3(1.6mA/V^2)}} = 1.12V,$$

$$V_{OL} = V_{DD} - V_{TO} - \sqrt{(V_{DD} - V_{TO})^2 - \left(\frac{K_L}{K_O}\right)V_{TL}^2}, \text{ and}$$

$$= 5V - 0.6V - \sqrt{(5V - 0.6V)^2 - \left(\frac{2.0mA/V^2}{1.6mA/V^2}\right)(-0.4V)^2} = 0.023V$$

$$V_{OH} = V_{DD} = 5V.$$

b. The SPICE results are shown in Figure 8.41.

 


Figure 8.41.

c. From the SPICE results, the critical voltages are $V_{OH} = 5.0V$, $V_{OL} = 0.023V$, $V_{IL} = 0.88V$, and

$$V_{IH} = 1.12V.$$

P8.9. Consider the NMOS gate of Figure 8.38.

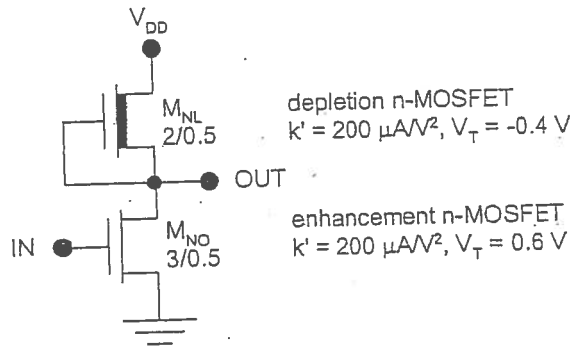


Figure 8.38.

- a. Using hand calculations, calculate and plot the DC power dissipation versus the supply voltage.
- b. Repeat using SPICE. Plot the results together on one graph for comparison.

Solution.

a. For the pull-up device,

$$K_L = \left(\frac{2 \mu\text{m}}{0.5 \mu\text{m}} \right) 200 \mu\text{A}/\text{V}^2 = 0.8 \text{mA}/\text{V}^2.$$

The dissipation is given by

$$P_{DC} \approx \frac{P_H + P_L}{2} = \frac{K_L V_{DD} V_{TL}^2}{4} = \frac{(0.8 \text{mA}/\text{V}^2)(V_{DD})(-0.4 \text{V})^2}{4} = 0.032 \text{mW}/\text{V}(V_{DD}).$$

b. The dissipation was determined as a function of the supply voltage in PSPICE using a DC sweep and a current probe. The calculated and PSPICE results coincide as shown in Figure 8.42.

 


Figure 8.42.

P8.10. Consider the NMOS gate shown in Figure 8.39.

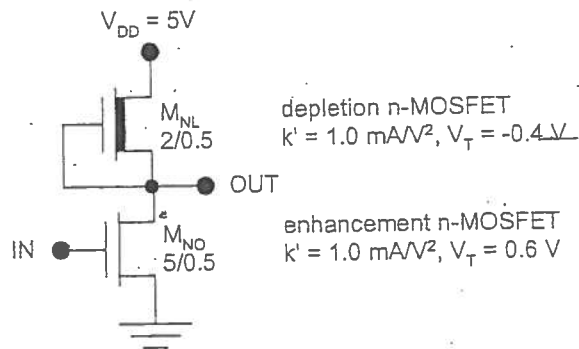


Figure 8.39.

- From the information given, estimate the oxide thickness used in the transistors.
- Calculate the approximate input capacitance for the inverter.
- Estimate the maximum fan-out if $t_{p,max} = 10 \text{ ns}$.

Solution.

- The oxide thickness is

$$t_{ox} = \frac{(580 \text{ cm}^2 \text{ V}^{-1} \text{ s}^{-1})(3.9)(8.85 \times 10^{-14} \text{ F/cm})}{1 \text{ mA/V}^2} = 2 \text{ nm}$$

b. The input capacitance for the inverter is

$$C_{IN} = \frac{(5 \times 10^{-4} \text{ cm})(0.5 \times 10^{-4} \text{ cm})(3.9)(8.85 \times 10^{-14} \text{ F/cm})}{20 \times 10^{-8} \text{ cm}} = 43 \text{ fF}$$

c. If $t_{pMAX} = 10 \text{ ns}$ then the maximum fan-out is given by

$$N_{MAX} \leq \frac{(4 \text{ mA/V}^2)(0.4 \text{ V})^2(10^{-8} \text{ s})}{(5 \text{ V})(43 \text{ fF})} = 30, \text{ or}$$

$$N_{MAX} = 30.$$

P8.11. Consider depletion loaded NMOS with $V_{DD} = 5 \text{ V}$, $V_{TO} = 0.5 \text{ V}$, $V_{TL} = -0.6 \text{ V}$, and $t_{ox} = 18 \text{ nm}$. All devices have $0.5 \mu\text{m}$ gate lengths. Choose the W_O/W_L ratio such that $V_{OL} = 25 \text{ mV}$.

Solution. The output low voltage is given by

$$\begin{aligned} V_{OL} &= V_{DD} - V_{TO} - \sqrt{(V_{DD} - V_{TO})^2 - \left(\frac{K_L}{K_O}\right)V_{TL}^2} \\ &= 5 \text{ V} - 0.5 \text{ V} - \sqrt{(5 \text{ V} - 0.5 \text{ V})^2 - \left(\frac{K_L}{K_O}\right)(-0.6 \text{ V})^2} = 0.025 \text{ V} \end{aligned}$$

Therefore the ratio of the device transconductance parameters should be

$$\begin{aligned} \frac{K_L}{K_O} &= \frac{(V_{DD} - V_{TO})^2 - (V_{DD} - V_{TO} - V_{OL})^2}{V_{TL}^2} \\ &= \frac{(5 \text{ V} - 0.5 \text{ V})^2 - (5 \text{ V} - 0.5 \text{ V} - 0.025 \text{ V})^2}{(-0.6 \text{ V})^2} = 0.62 \end{aligned}$$

The ratio of the device widths should be

$$\frac{W_O}{W_L} = \frac{K_O}{K_L} = \frac{1}{0.62} = 1.61.$$

P8.12. Consider depletion loaded NMOS with $V_{DD} = 3.3V$, $V_{TO} = 0.5V$, $V_{TL} = -0.3V$, and $t_{ox} = 10 \text{ nm}$. All devices have $0.35 \mu\text{m}$ gate lengths. Design the transistors for the inverter (choose W_O and W_L) such that $V_{OL} = 20 \text{ mV}$ and the average DC dissipation is 2 mW .

Solution. The DC power dissipation is given by

$$P_{DC} \approx \frac{P_H + P_L}{2} = \frac{K_L V_{DD} V_{TL}^2}{4} = 2 \text{ mW}.$$

Therefore the value of K_L can be chosen as

$$K_L = \frac{(4)(2 \text{ mW})}{(3.3V)(-0.3V)^2} = 27 \text{ mA/V}^2.$$

The output low voltage is given by

$$\begin{aligned} V_{OL} &= V_{DD} - V_{TO} \pm \sqrt{(V_{DD} - V_{TO})^2 - \left(\frac{K_L}{K_O}\right) V_{TL}^2} \\ &= 3.3V - 0.5V \pm \sqrt{(3.3V - 0.5V)^2 - \left(\frac{K_L}{K_O}\right) (-0.3V)^2} = 0.020V \end{aligned}$$

Therefore,

$$\frac{K_L}{K_O} = 1.24 \text{ and}$$

$$K_O = 22 \text{ mA/V}^2.$$

The process transconductance parameter is

$$k'_N = \frac{(580 \text{ cm}^2 / \text{Vs})(3.9)(8.85 \times 10^{-14} \text{ F./cm})}{100 \times 10^{-8} \text{ cm}} = 0.200 \text{ mA/V}^2.$$

The widths for the devices should therefore be:

$$W_L = \left(\frac{27 \text{ mA/V}^2}{0.20 \text{ mA/V}^2} \right) 0.35 \mu\text{m} = 47 \mu\text{m}, \text{ and}$$

$$W_O = \left(\frac{22 \text{ mA/V}^2}{0.20 \text{ mA/V}^2} \right) 0.35 \mu\text{m} = 38 \mu\text{m}.$$

P8.13. Consider depletion loaded NMOS with $V_{DD} = 3.3\text{V}$, $V_{TO} = 0.5\text{V}$, $V_{TL} = -0.3\text{V}$, and $t_{ox} = 10 \text{ nm}$. All devices have $0.35 \mu\text{m}$ gate lengths. Design the transistors for the inverter (choose W_O and W_L) such that $V_{OL} = 20 \text{ mV}$ and $t_p \leq 10 \text{ ns}$ with $C_L = 15 \text{ pF}$. (Consider the worst case propagation delay.)

Solution.

$$\begin{aligned} V_{OL} &= V_{DD} - V_{TO} \pm \sqrt{(V_{DD} - V_{TO})^2 - \left(\frac{K_L}{K_O} \right) V_{TL}^2} \\ &= 3.3\text{V} - 0.5\text{V} \pm \sqrt{(3.3\text{V} - 0.5\text{V})^2 - \left(\frac{K_L}{K_O} \right) (-0.3\text{V})^2} = 0.020\text{V} \end{aligned}$$

$$\frac{K_L}{K_O} = 1.24$$

$$t_{PLH} = \frac{V_{DD} C_L}{K_L V_{TL}^2} = \frac{(3.3\text{V})(15 \text{ pF})}{1.24 K_O (-0.3\text{V})^2} = \frac{0.44 \text{ nsA/V}^2}{K_O}$$

The high to low propagation delay is

$$t_{PHL} \approx \frac{V_{DD} C_L}{K_O (V_{DD} - V_{TO})^2} = \frac{(3.3\text{V})(15 \text{ pF})}{K_O (3.3\text{V} - 0.5\text{V})^2} = \frac{0.0063 \text{ nsA/V}^2}{K_O}$$

Considering the worst case, which is t_{PLH} ,

$$K_O \geq \frac{0.44 \text{ nsA/V}^2}{10 \text{ ns}} = 0.044 \text{ A/V}^2$$