

EG-EE445

1. An inverter has a measured delay of 2ns.

- a- If five identical delays are connected in series as shown in Figure 1, what is the delay from a to b?

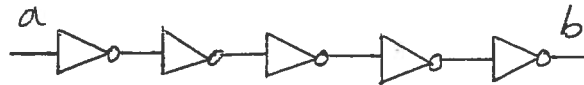


Figure 1

- b- If the a and b are connected together as shown in Figure 2 such that the voltage at a will now oscillate like a clock,

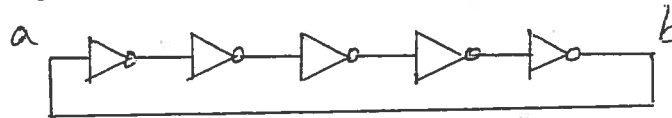


Figure 2

- (i) what is the period of oscillation?  
 (ii) What is the frequency of oscillation?

2. A step input from 0 V to 1.2 V is applied to the RC circuit of Figure 3. Calculate the time required for the voltage across the capacitor to: a) reach 0.6 V, b) reach 1.2 V, c) go from 10% to 90% of 1.2 V?

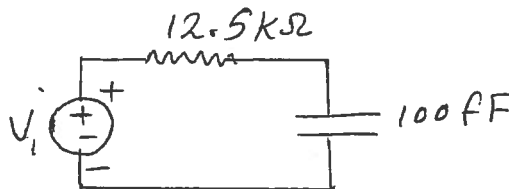


Figure 3

3. The uniform areal density of defects for a CMOS fabrication process is  $0.0063\text{ mm}^{-2}$ . Estimate the yield for  $9 \times 12\text{ mm}$  chips.

4. The uniform areal density of defects for a CMOS fabrication process is  $0.0014\text{ mm}^{-2}$ . Estimate the maximum economically viable chip size.

5. When a type of integrated circuit is tested at  $200^\circ\text{C}$ , 10% of the circuits fail within 1000 h with  $V_{DD} = 1.65\text{ V}$ . Estimate the 10% lifetime at  $175^\circ\text{C}$  and 1.65 V supply voltage, assuming  $E_a = 1.0\text{ eV}$ . Repeat for  $100^\circ\text{C}$ .

# EE445 homework 1 - Solutions

Q1 - a) delay (a-b) =  $5 \times 2 \text{ nsec} = 10 \text{ nsec}$

b) part (i) -  $f = \frac{1}{M(t_{PHL} + t_{PLH})}$

$$t_p = \frac{t_{PHL} + t_{PLH}}{2} \Rightarrow f = \frac{1}{M \times 2 t_p}$$

$$M = 5 \Rightarrow f = \frac{1}{10 t_p} = \frac{1}{10 \times 2 \text{ nsec}} = \frac{1}{20 \text{ nsec}}$$

$$\therefore T = 20 \text{ nsec}$$

part (ii):  $f = \frac{1}{20 \text{ nsec}} = 50 \text{ MHz}$

Q2 -

a)  $V_0 = V(1 - e^{-t/RC}) = 1.2 (1 - e^{-t / (2.5 \times 10^{-3} \times 100 \times 10^{-15})})$

$$\therefore V_0 = 1.2 (1 - e^{-8 \times 10^8 t})$$

$$\text{if } V_0 = 0.6 \text{ V} \Rightarrow 0.6 = 1.2 (1 - e^{-8 \times 10^8 t_1})$$

$$\therefore t_1 = 0.866 \text{ nsec}$$

b) for  $V_0 = 1.2 \Rightarrow t = \infty$

c) 
$$\begin{cases} 1 - e^{-8 \times 10^8 t'} = 0.1 \Rightarrow e^{-8 \times 10^8 t'} = 0.9 \\ 1 - e^{-8 \times 10^8 t''} = 0.9 \Rightarrow e^{-8 \times 10^8 t''} = 0.1 \end{cases}$$

$$\therefore \frac{e^{-8 \times 10^8 (t' - t'')}}{e} = 9 \Rightarrow (t'' - t') = t_r = \frac{\ln 9}{8 \times 10^8} = 2.7$$

Q3

$$Y = \exp(-D_0 A) = \exp\left\{-(9 \text{ mm})(12 \text{ mm})(0.0063 \text{ mm}^{-2})\right\} = 50\%$$

Q4

$$Y = e^{-D_0 A} \geq 0.95$$

$$\therefore A \leq \frac{-\ln(0.95)}{D_0} = \frac{0.051}{0.0014 \text{ mm}^{-2}}$$

$$\therefore A \leq 36 \text{ mm}^2 = 0.36 \text{ cm}^2$$

Q5

At  $200^\circ\text{C}$ , the acceleration factor with respect to  $100^\circ\text{C}$  is:

$$A_{200} = \exp\left\{\frac{1 \text{ eV}}{8.7 \times 10^{-5} \text{ eV/K}} \left(\frac{1}{100+273} - \frac{1}{200+273}\right)\right\} = 675$$

At  $175^\circ\text{C}$ , the acceleration factor with respect to  $100^\circ\text{C}$  is:

$$A_{175} = \exp\left[\frac{1 \text{ eV}}{8.7 \times 10^{-5} \text{ eV/K}} \left(\frac{1}{100+273} - \frac{1}{175+273}\right)\right] = 174$$

$\therefore$  The lifetime at  $100^\circ\text{C}$  is

$$A_{200}(675) = 675,000 \text{ hrs}$$

$$\therefore \text{The lifetime at } 175^\circ\text{C} \text{ is: } 675,000/174 = 3900 \text{ hrs}$$